



---

**HY313X**  
**Configurations**

## Table of Contents

<b>1. DCMV .....</b>	<b>6</b>
1.1. Input Network Configuration.....	6
1.2. DC50mV Measurement Network Configuration.....	7
1.3. DC500mV Measurement Network Configuration.....	8
<b>2. ACMV .....</b>	<b>9</b>
2.1. Input Network Configuration.....	9
2.2. AC Low Pass Filter Measurement Network Configuration.....	10
2.3. AC50mV Measurement Network Configuration .....	10
2.4. AC500mV Measurement Network Configuration .....	11
<b>3. DCV .....</b>	<b>12</b>
3.1. 5V Input Network Configuration .....	12
3.2. 50V Input Network Configuration .....	13
3.3. 500V Input Network Configuration .....	14
3.4. 1000V Input Network Configuration .....	15
3.5. DC5V~1000V Measurement Network Configuration .....	16
<b>4. ACV .....</b>	<b>17</b>
4.1. AC Low Pass Filter Measurement Network Configuration.....	17
4.2. 5V Input Network Configuration .....	18
4.3. 50V Input Network Configuration .....	19
4.4. 500V Input Network Configuration .....	20
4.5. 1000V Input Network Configuration .....	21
4.6. AC5V~1000V Measurement Network Configuration .....	22

# **HY313X**

## **Configurations**

---



<b>5. CAPACITOR.....</b>	<b>23</b>
5.1. 50-500nF (Constant Voltage Charge/Discharge Measurement).....	24
5.2. 5uF-50uF (Constant Current Charge/Discharge Measurement) .....	25
5.3. 500uF(Charge) .....	26
5.4. 5mF-50mF(Charge).....	27
5.5. 500uF~50mF Measurement Network Configuration.....	28
5.6. Discharge (500uF~50mF) .....	29
<b>6. RESISTOR .....</b>	<b>31</b>
6.1. 50ohm/500ohm Input Network Configuration .....	33
6.2. 5K ohm Input Network Configuration .....	34
6.3. 50ohm Measurement Network Configuration .....	35
6.4. 500 ohm~50K ohm Measurement Network Configuration.....	36
6.5. 50Kohm Input Network Configuration .....	37
6.6. 500Kohm Input Network Configuration .....	38
6.7. 5M ohm Input Network Configuration.....	39
6.8. 50Mohm Input Network Configuration.....	40
6.9. 500Kohm~50Mohm Measurement Network Configuration.....	41
<b>7. DIODE .....</b>	<b>42</b>
7.1. Diode Input Network Configuration .....	42
7.2. Diode Measurement Network Configuration .....	43
<b>8. CONTINUITY.....</b>	<b>44</b>
<b>9. CURRENT .....</b>	<b>45</b>
9.1. DC 50mA .....	45

# **HY313X**

## **Configurations**

---



9.2.	DC 500mA.....	46
9.3.	AC 50mA.....	47
9.4.	AC 500mA.....	48
<b>10.</b>	<b>FREQUENCY.....</b>	<b>49</b>
10.1.	Voltage input.....	49
10.2.	CNT input .....	50
<b>11.</b>	<b>REVISION HISTORY .....</b>	<b>51</b>

Attention :

1. HYCON Technology Corp. reserves the right to change the content of this datasheet without further notice. For most up-to-date information, please constantly visit our website:  
<http://www.hycontek.com>.
2. HYCON Technology Corp. is not responsible for problems caused by figures or application circuits narrated herein whose related industrial properties belong to third parties.
3. Specifications of any HYCON Technology Corp. products detailed or contained herein stipulate the performance, characteristics, and functions of the specified products in the independent state. We does not guarantee of the performance, characteristics, and functions of the specified products as placed in the customer's products or equipment. Constant and sufficient verification and evaluation is highly advised.
4. Please note the operating conditions of input voltage, output voltage and load current and ensure the IC internal power consumption does not exceed that of package tolerance. HYCON Technology Corp. assumes no responsibility for equipment failures that resulted from using products at values that exceed, even momentarily, rated values listed in products specifications of HYCON products specified herein.
5. Notwithstanding this product has built-in ESD protection circuit, please do not exert excessive static electricity to protection circuit.
6. Products specified or contained herein cannot be employed in applications which require extremely high levels of reliability, such as device or equipment affecting the human body, health/medical equipments, security systems, or any apparatus installed in aircrafts and other vehicles.
7. Despite the fact that HYCON Technology Corp. endeavors to enhance product quality as well as reliability in every possible way, failure or malfunction of semiconductor products may happen. Hence, users are strongly recommended to comply with safety design including redundancy and fire-precaution equipments to prevent any accidents and fires that may follow.
8. Use of the information described herein for other purposes and/or reproduction or copying without the permission of HYCON Technology Corp. is strictly prohibited.


### 1. DCmV

Due to high ADC input impedance, it is easily to sense 50/60Hz signal of the air that leads to unstable reading value after the testing probe was connected. It is recommended to connect input  $10M\Omega$  to ground to reduce input impedance of DMM mV range.


The network configuration of 50mV and 500mV is similar. When measuring 50mV, it uses built-in OPA to amplify signal for 10 times then processing it in ADC.

Main function of chopper is to reduce DC Offset. When OPA measures DC, it is advised to open ADC1 Pre-Filter.


#### 1.1. Input Network Configuration

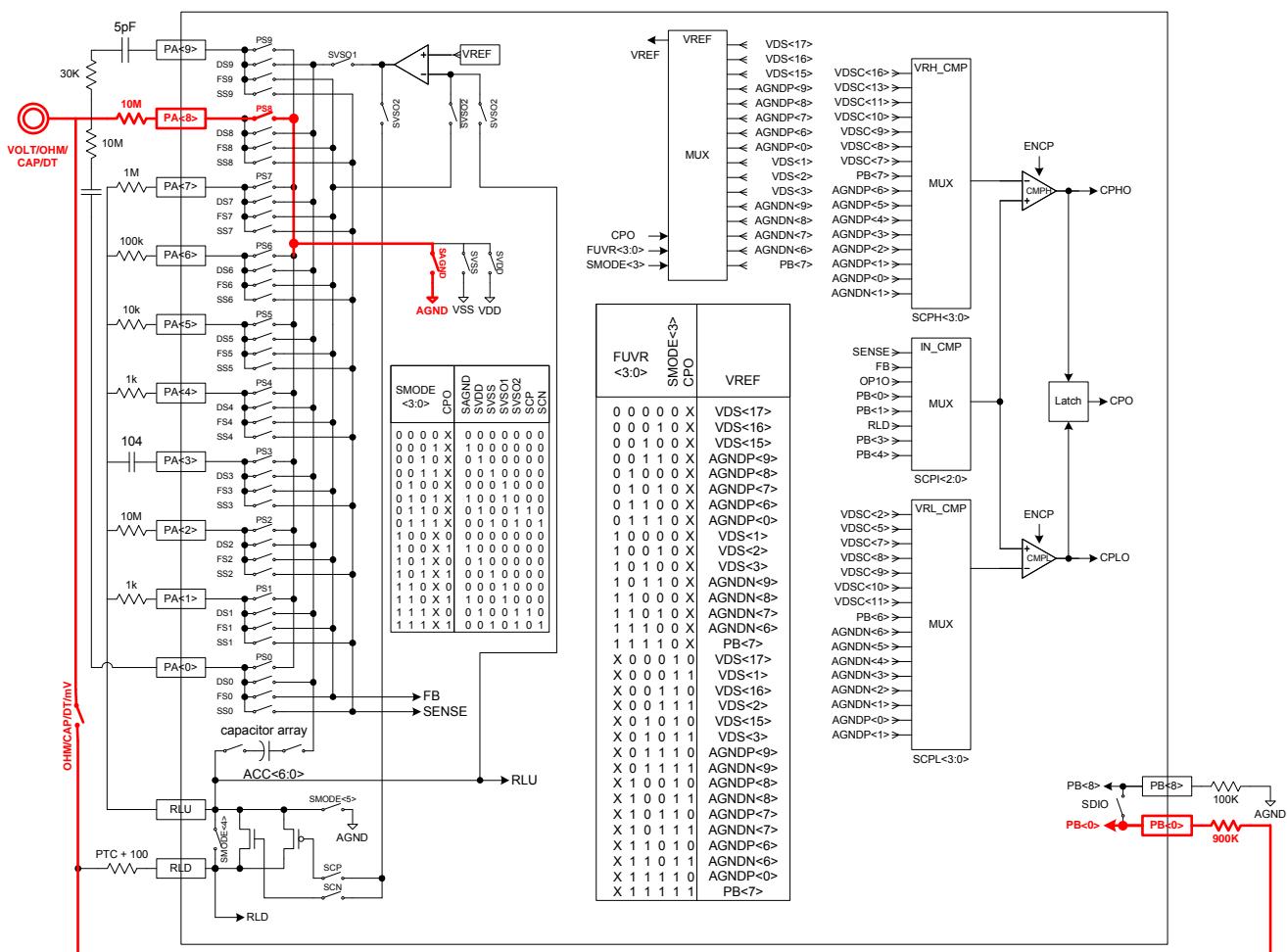
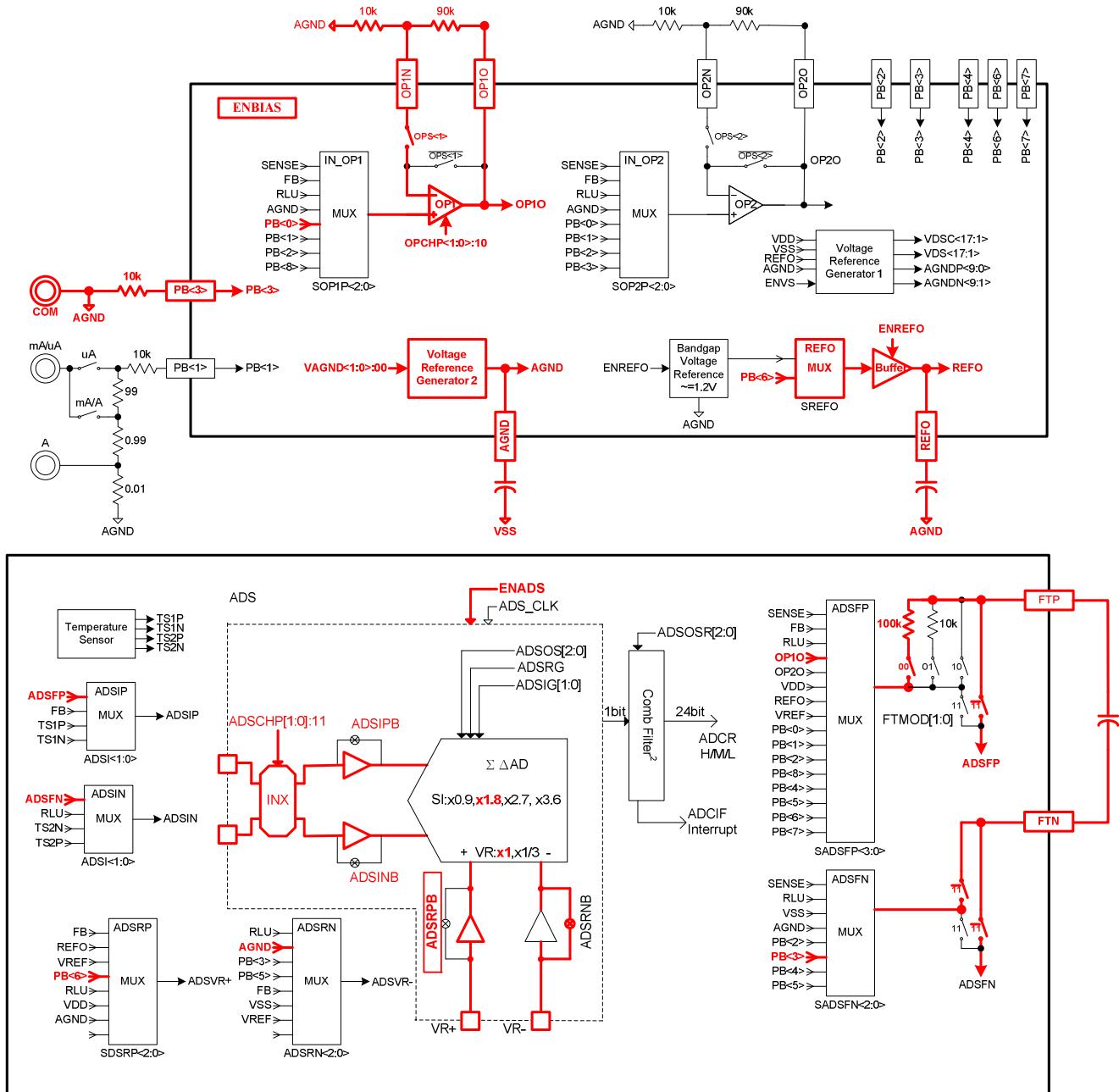
## 1.2. DC50mV Measurement Network Configuration


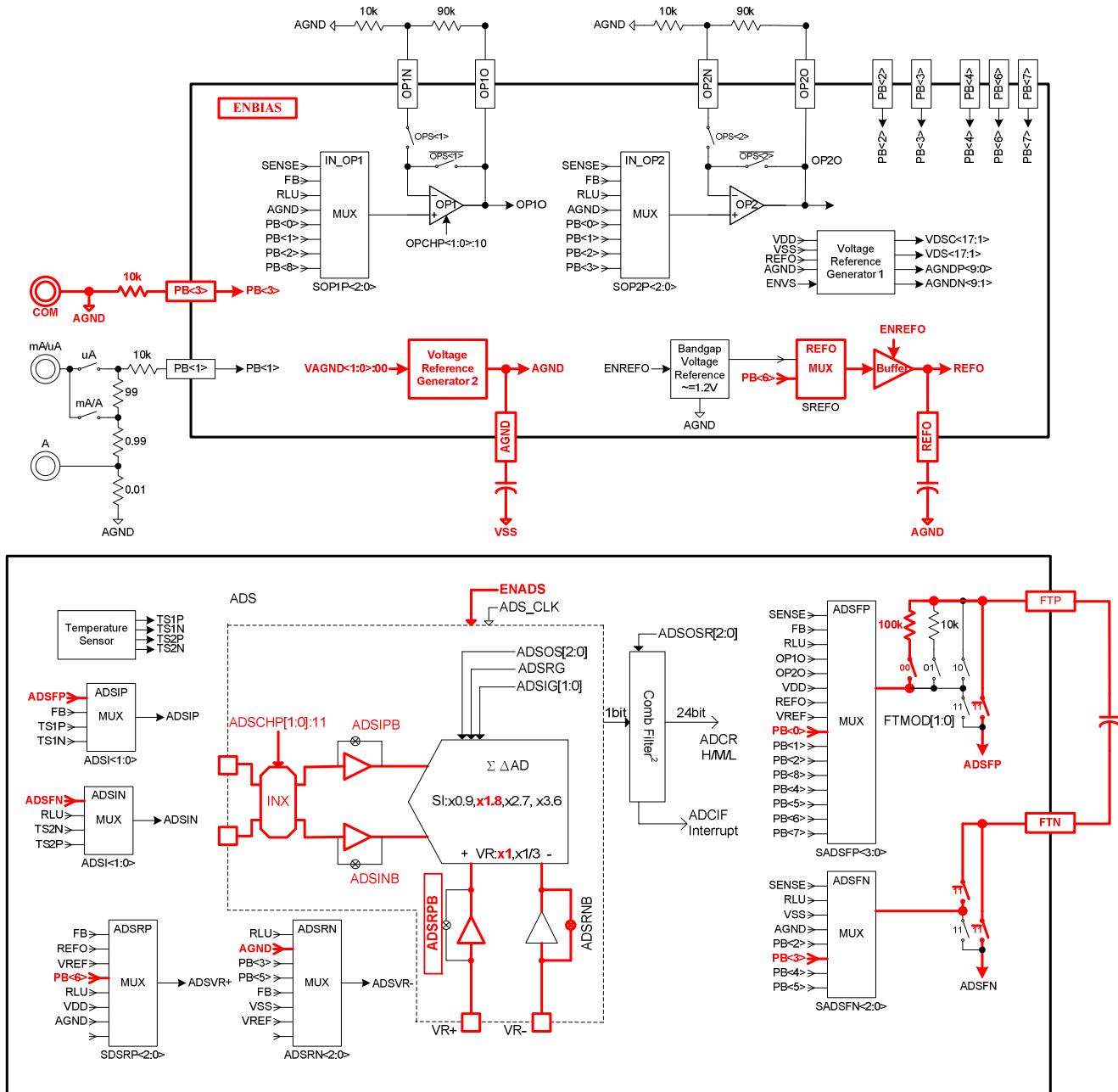
### 1.3. DC500mV Measurement Network Configuration




## 2. ACmV


Due to high ADC input impedance, it is easily to sense 50/60Hz signal of the air that leads to unstable reading value after the testing probe was connected. It is recommended to connect input  $10M\Omega$  to ground to reduce input impedance of DMM mV range.

The network configuration of 50mV and 500mV is similar. When measuring 50mV, it uses built-in OPA to amplify signal for 10 times then processing it in ADC.


### 2.1. Input Network Configuration

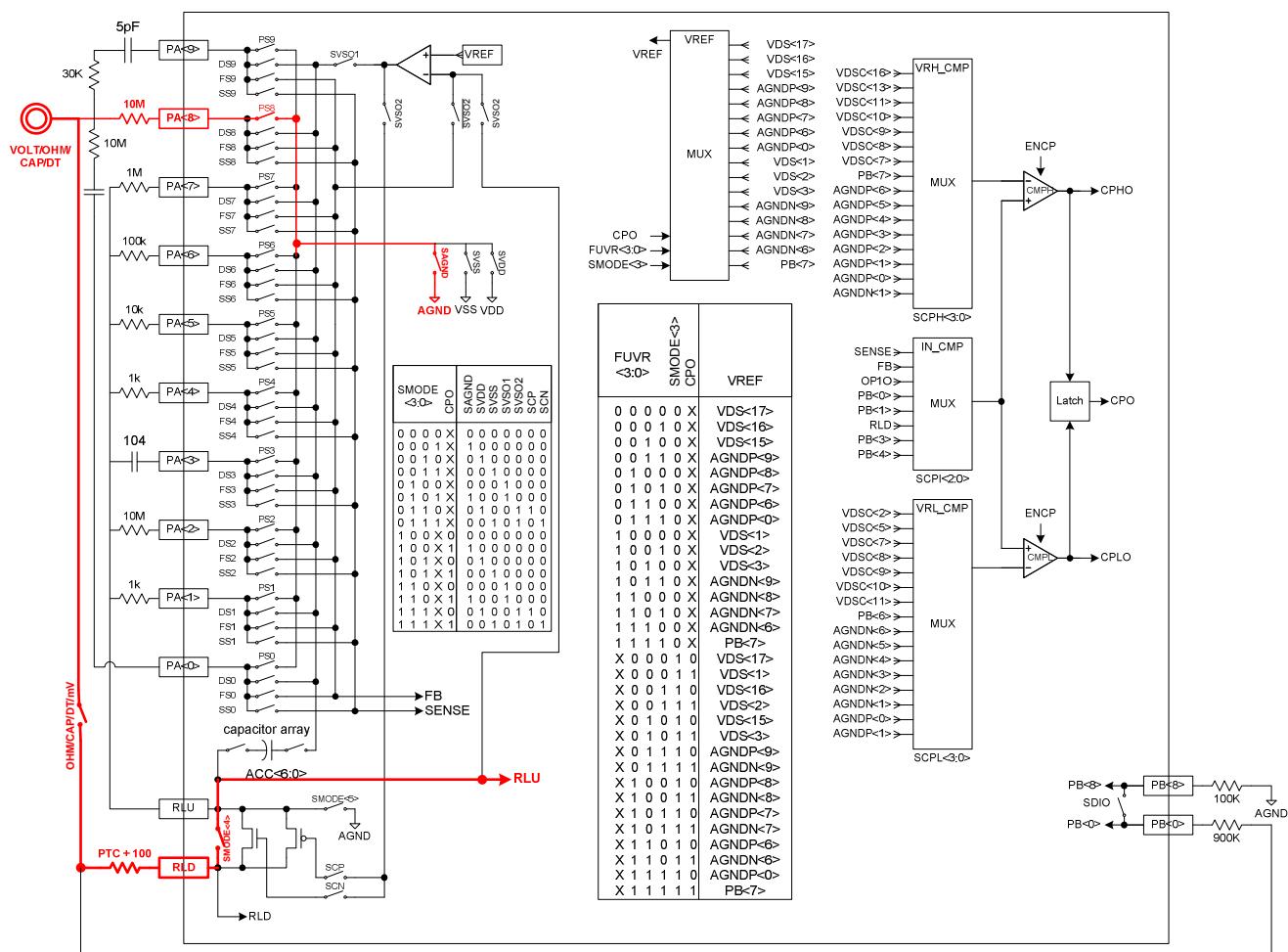

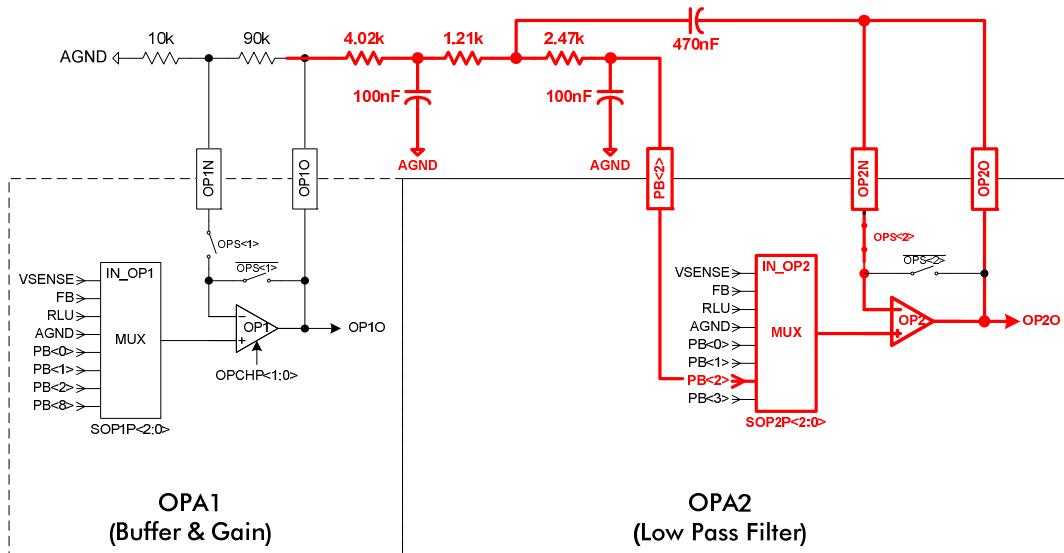
### 2.2. AC Low Pass Filter Measurement Network Configuration


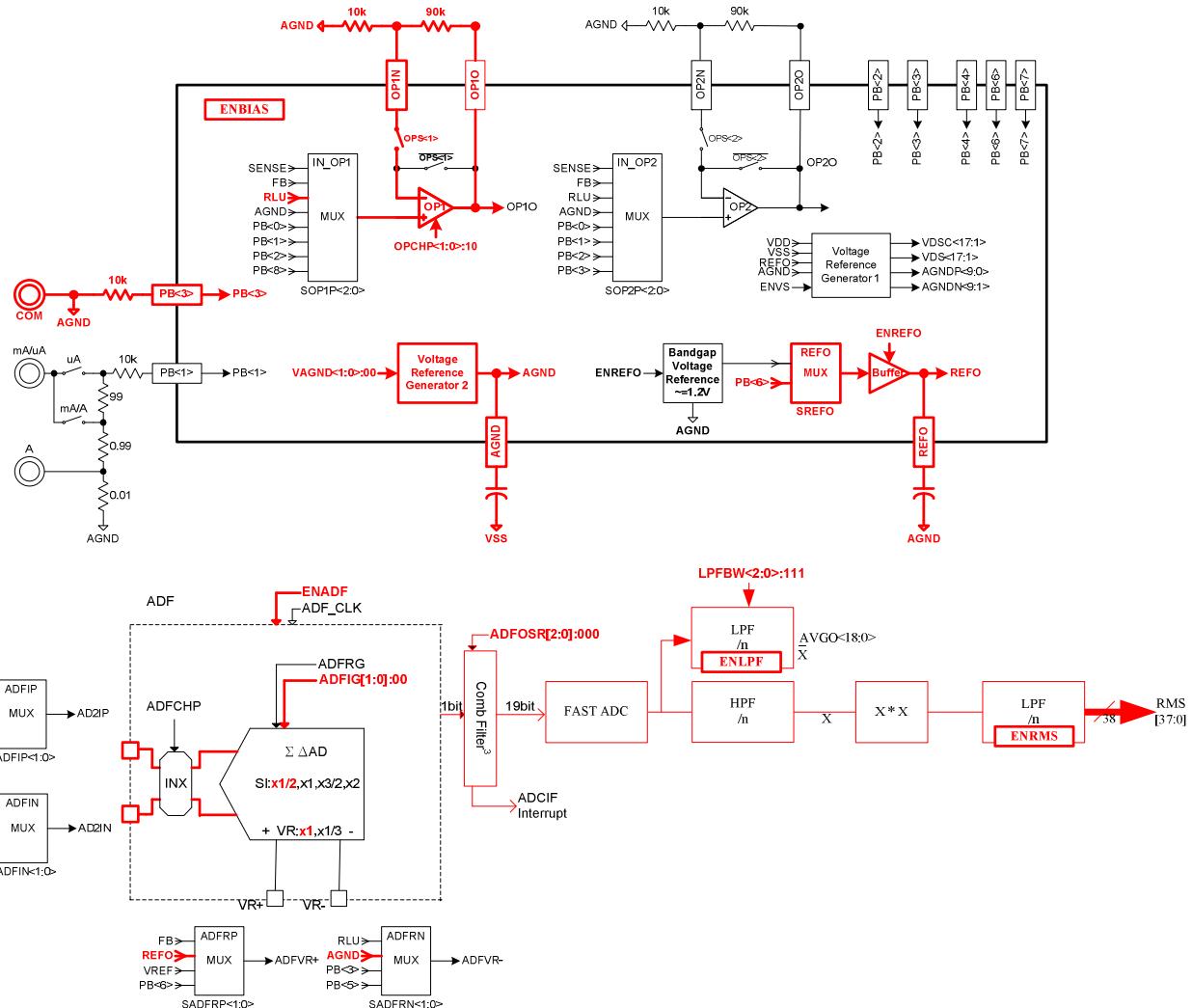
### 2.3. AC50mV Measurement Network Configuration


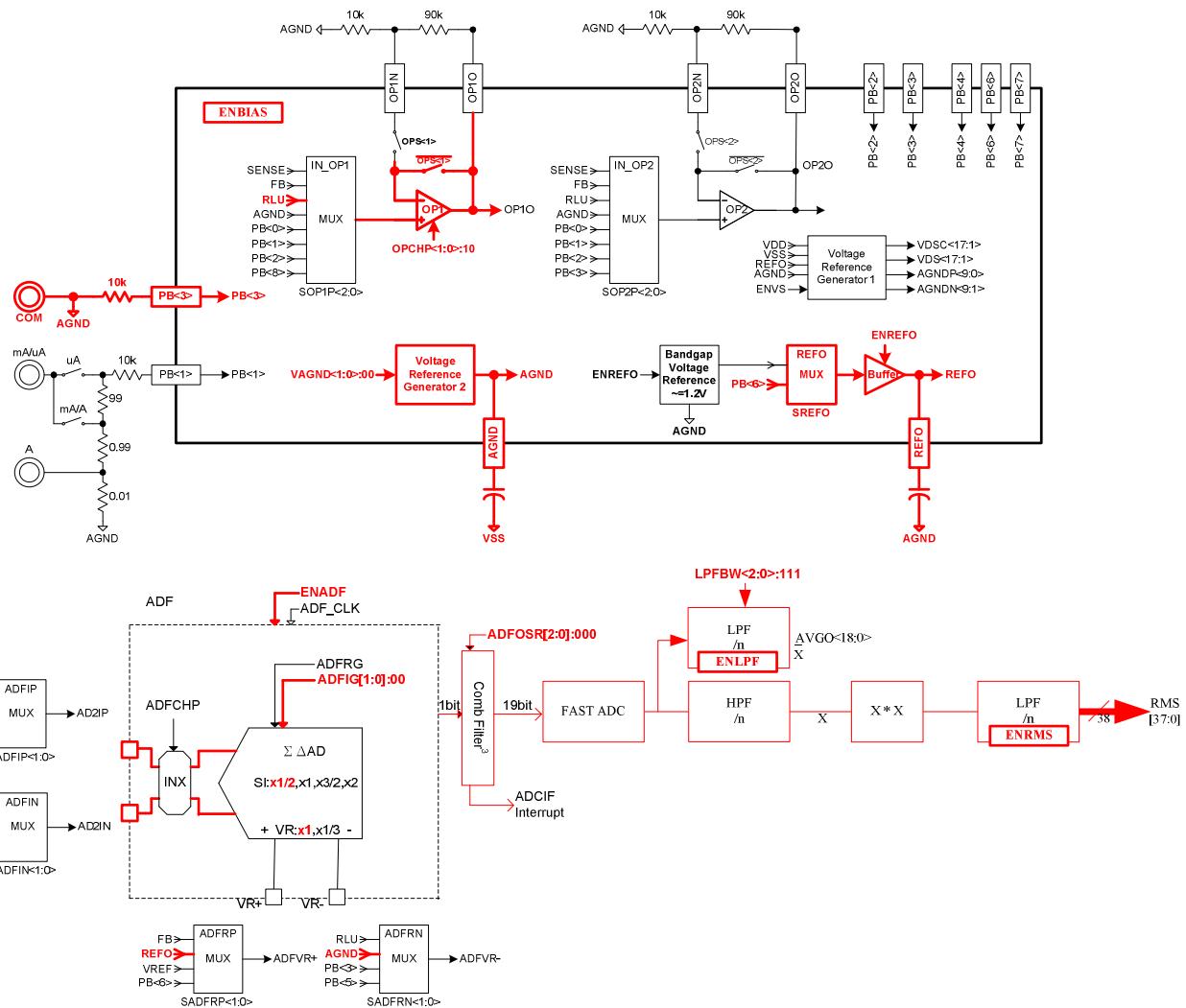
### 2.4. AC500mV Measurement Network Configuration



### **3. DCV**

30K $\Omega$  resistor and 5pF capacitor of the input end is for the use of ACV frequency compensation. When DCV is not in use, it is recommended to connect to ground and its input divider of voltage range is shown in below equation :

$$5V\_Range \Rightarrow V_{IN} \times \frac{1.111M\Omega}{10M\Omega + 1.111M\Omega} = \frac{V_{IN}}{10}$$


$$50V\_Range \Rightarrow V_{IN} \times \frac{101.01K\Omega}{10M\Omega + 101.01K\Omega} = \frac{V_{IN}}{100}$$

$$500V\_Range \Rightarrow V_{IN} \times \frac{10.01\text{K}\Omega}{10\text{M}\Omega + 10.01\text{K}\Omega} = \frac{V_{IN}}{1000}$$


$$1000V\_Range \Rightarrow V_{IN} \times \frac{1K\Omega}{10M\Omega + 1K\Omega} = \frac{V_{IN}}{10000}$$

HY313x has two sets OPA that can be used to amplify 10 times of signal, realizing 500mV measurement by collocating with 5V network configurations.

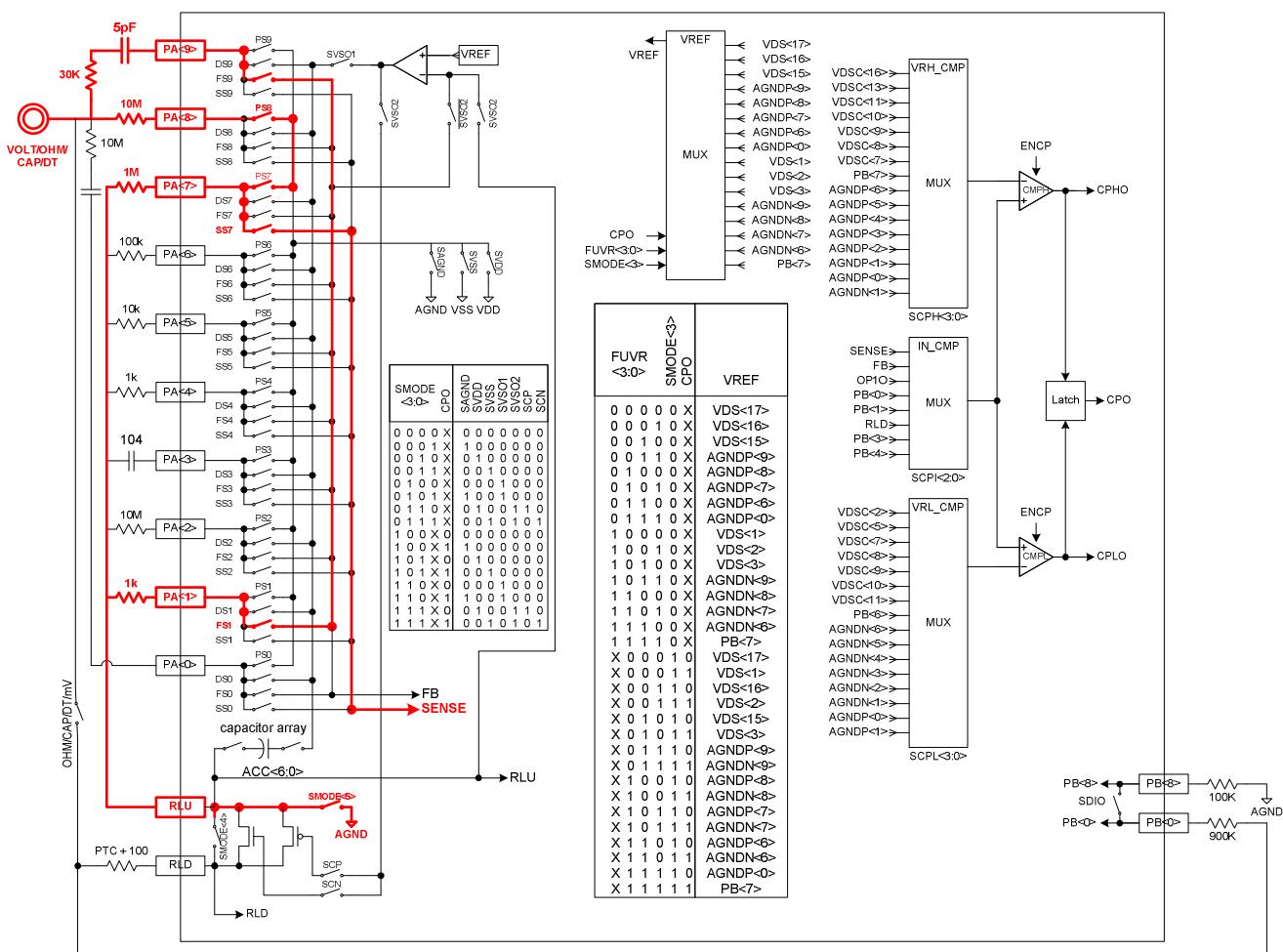
### **3.1. 5V Input Network Configuration**




### 3.2. 50V Input Network Configuration

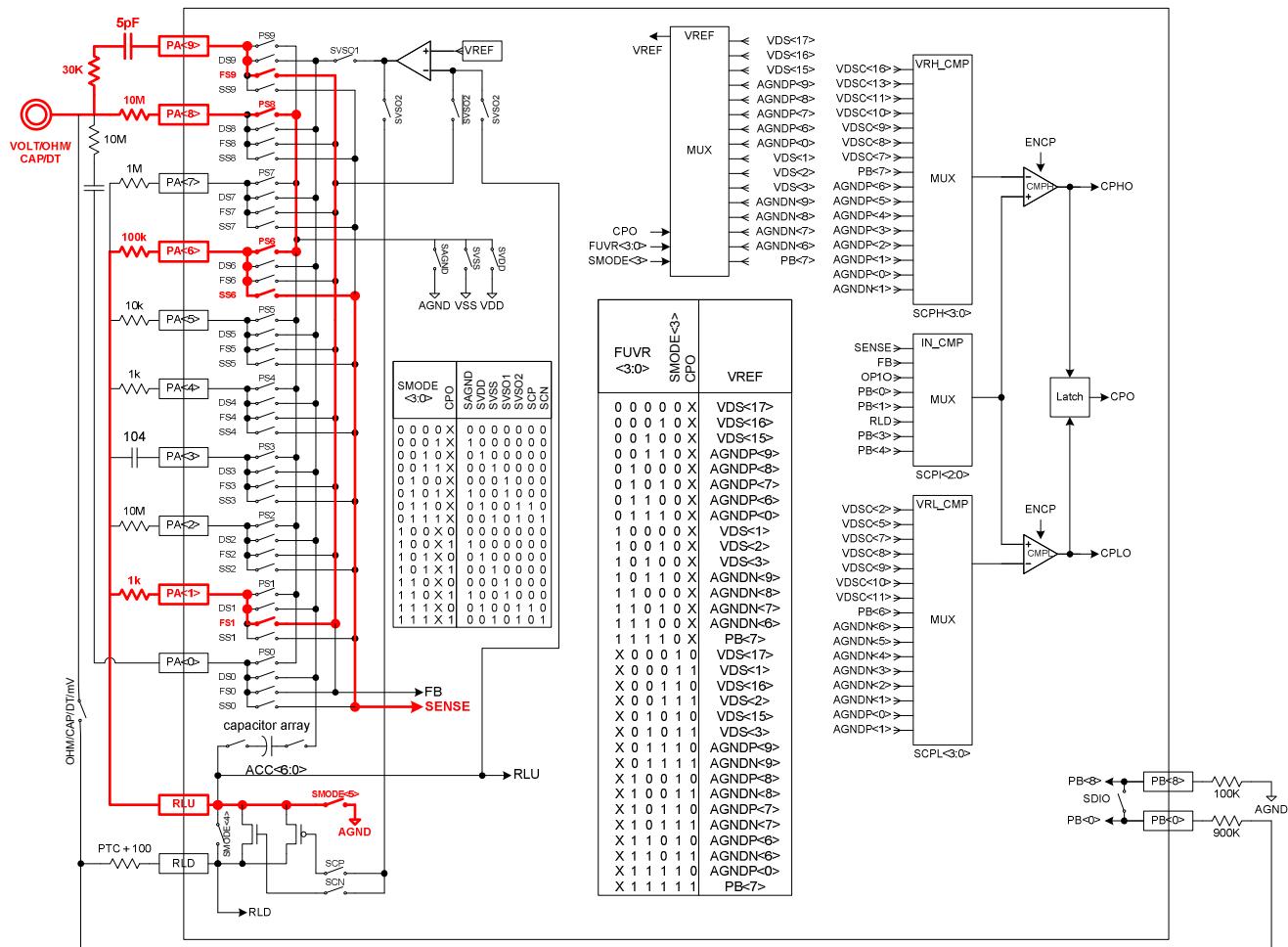
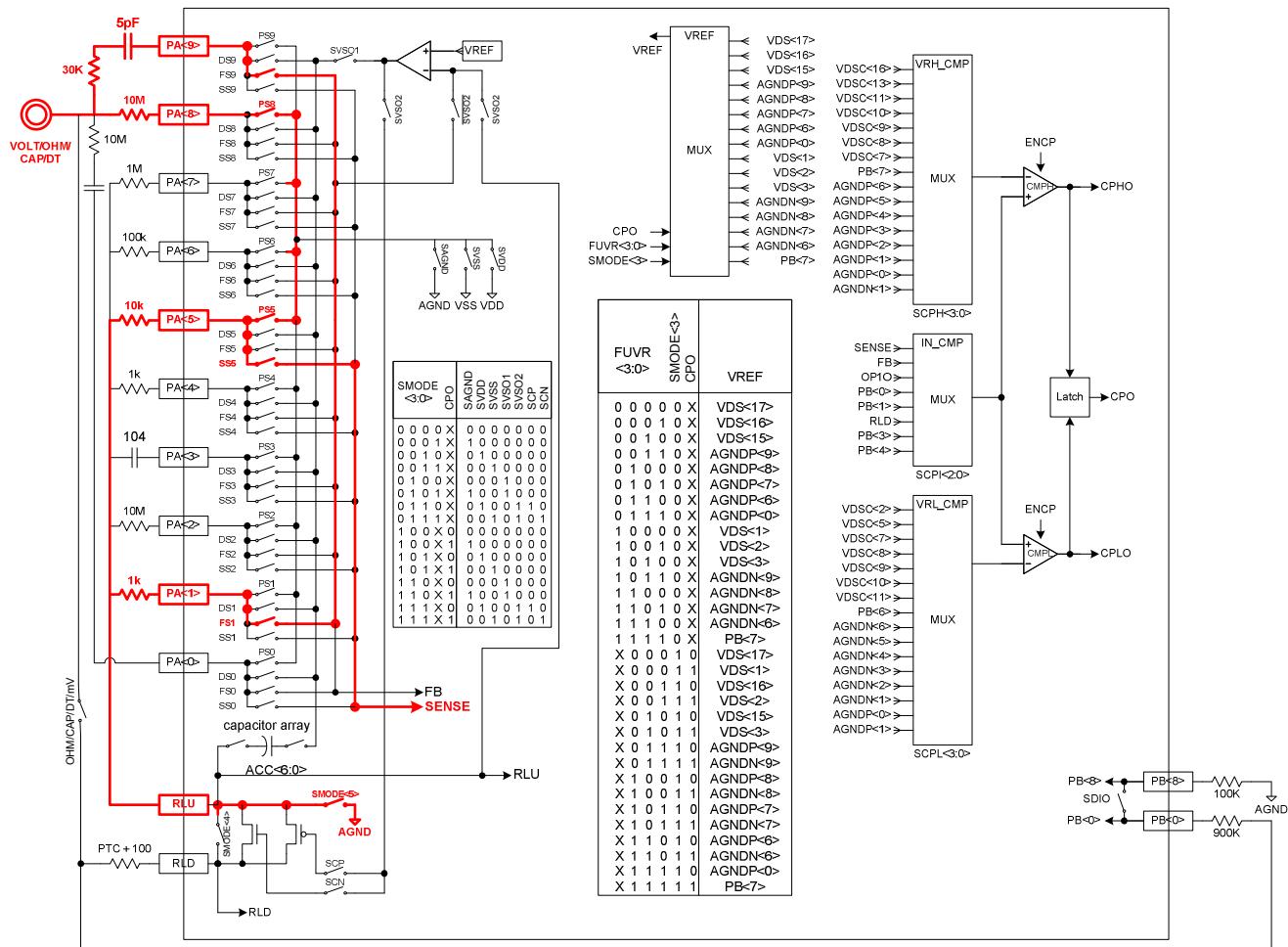
### 3.3. 500V Input Network Configuration




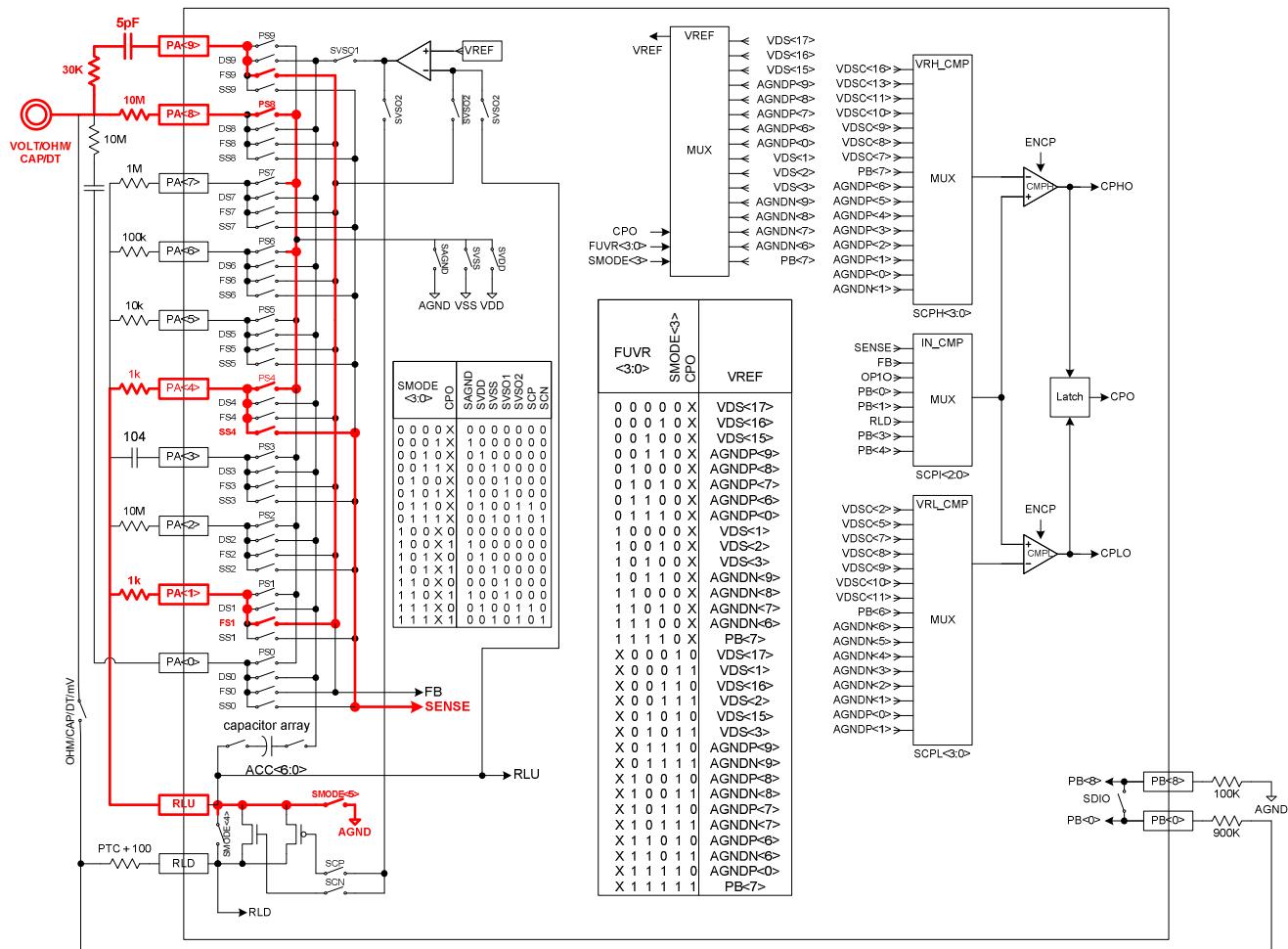
### 3.4. 1000V Input Network Configuration


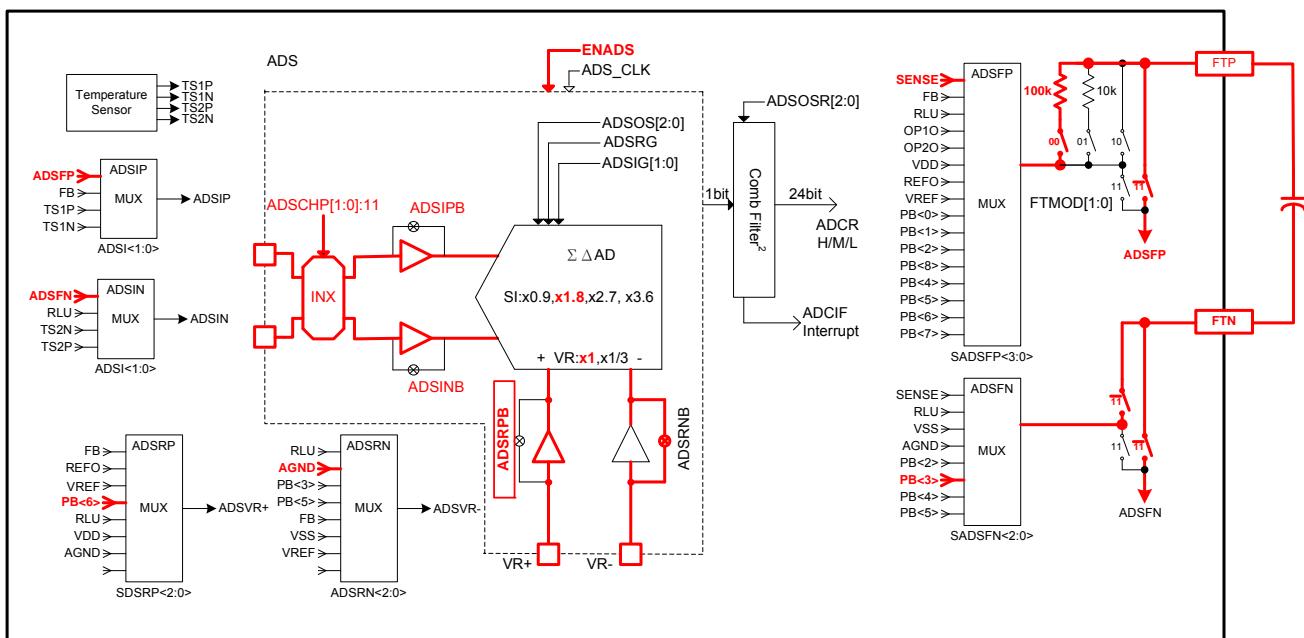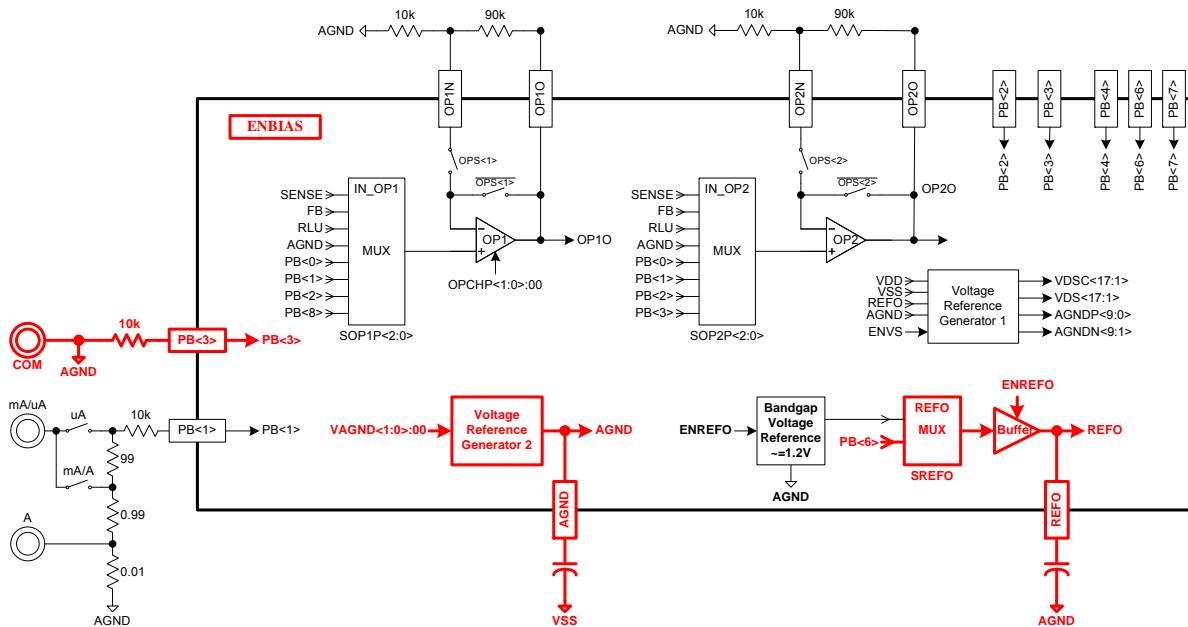
### 3.5. DC5V~1000V Measurement Network Configuration

Main function of Chopper is to reduce DC Offset.



### 4. ACV

30K $\Omega$  resistor and 5pF capacitor of the input end is to compensate ACV frequency.

When a part of ranges are not in use, it is recommended to connect to ground and its input divider of voltage range is shown in below equation :

$$5V\_Range \Rightarrow V_{IN} \times \frac{1.111M\Omega}{10M\Omega + 1.111M\Omega} = \frac{V_{IN}}{10}$$

$$50V\_Range \Rightarrow V_{IN} \times \frac{101.01K\Omega}{10M\Omega + 101.01K\Omega} = \frac{V_{IN}}{100}$$

$$500V\_Range \Rightarrow V_{IN} \times \frac{10.01K\Omega}{10M\Omega + 10.01K\Omega} = \frac{V_{IN}}{1000}$$


$$1000V\_Range \Rightarrow V_{IN} \times \frac{1K\Omega}{10M\Omega + 1K\Omega} = \frac{V_{IN}}{10000}$$

HY313x has two sets OPA that can be used to amplify 10 times of signal, realizing 500mV measurement by collocating with 5V network configurations.


Digital ACV bandwidth compensation capacitor equation is as follows :

$$\text{Capacitor array} = \sum_{n=0}^6 ACC< n > \times 2^n \times 0.2 pF$$

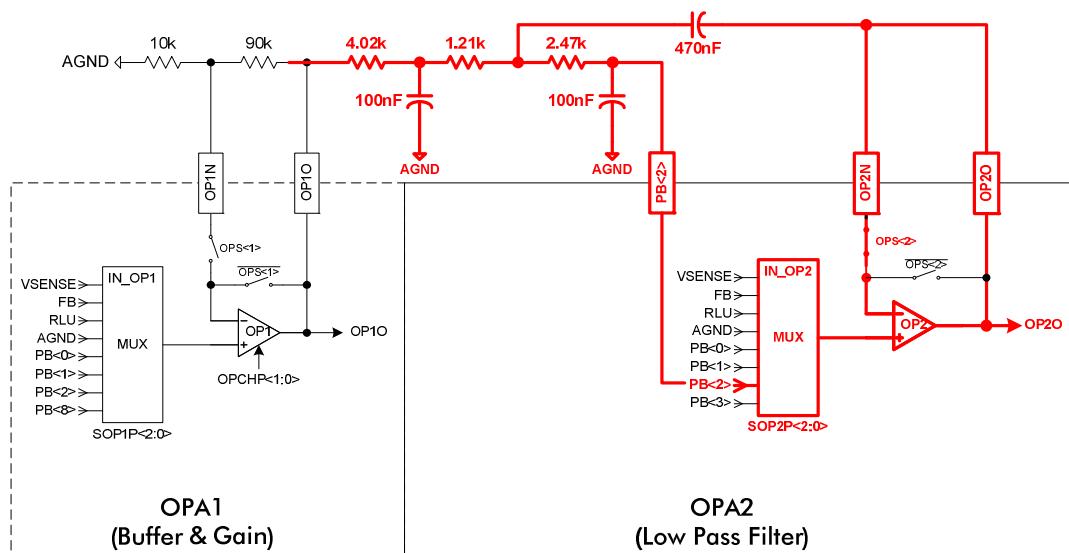
#### 4.1. AC Low Pass Filter Measurement Network Configuration




### 4.2. 5V Input Network Configuration

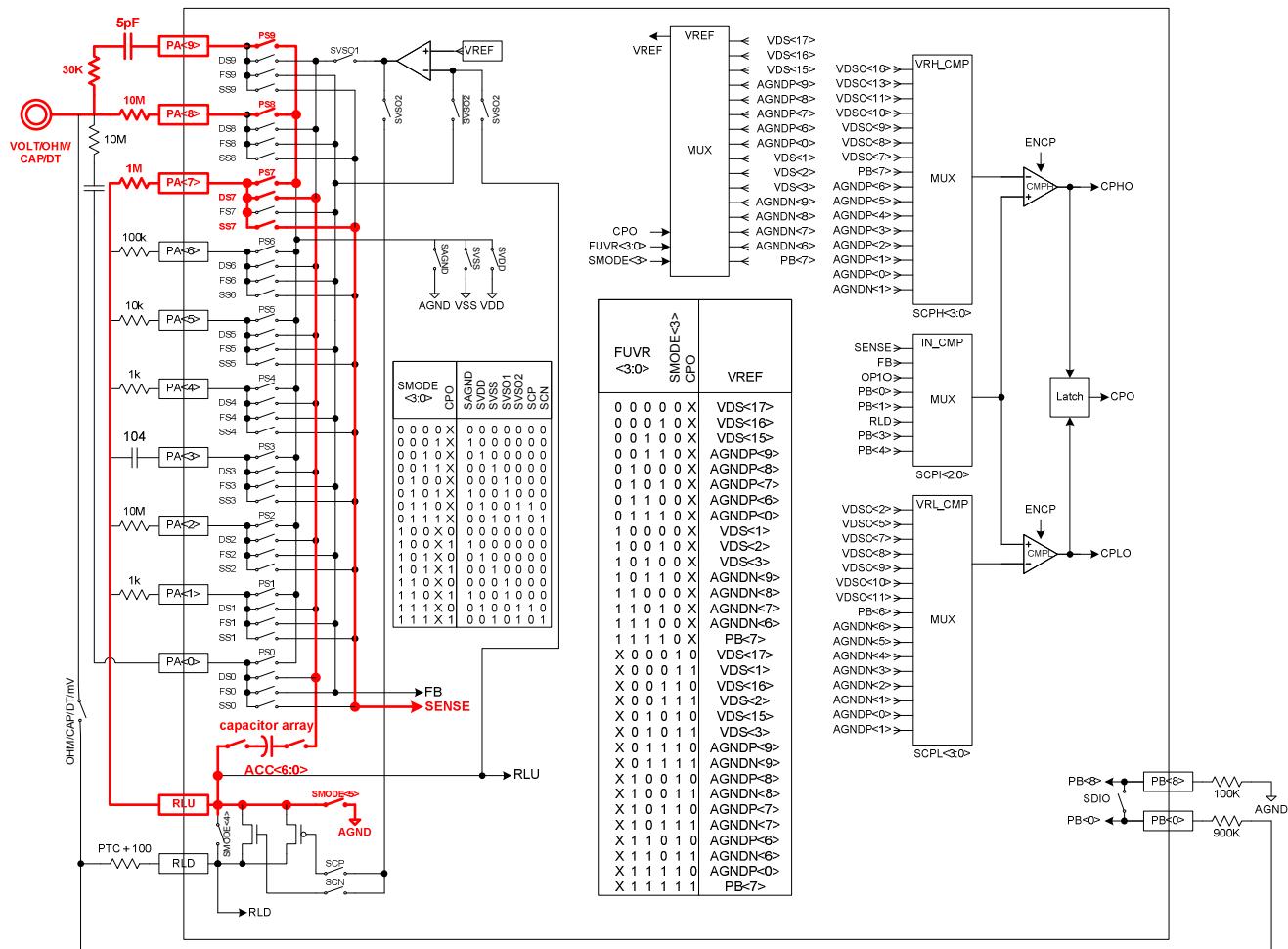


### 4.3. 50V Input Network Configuration

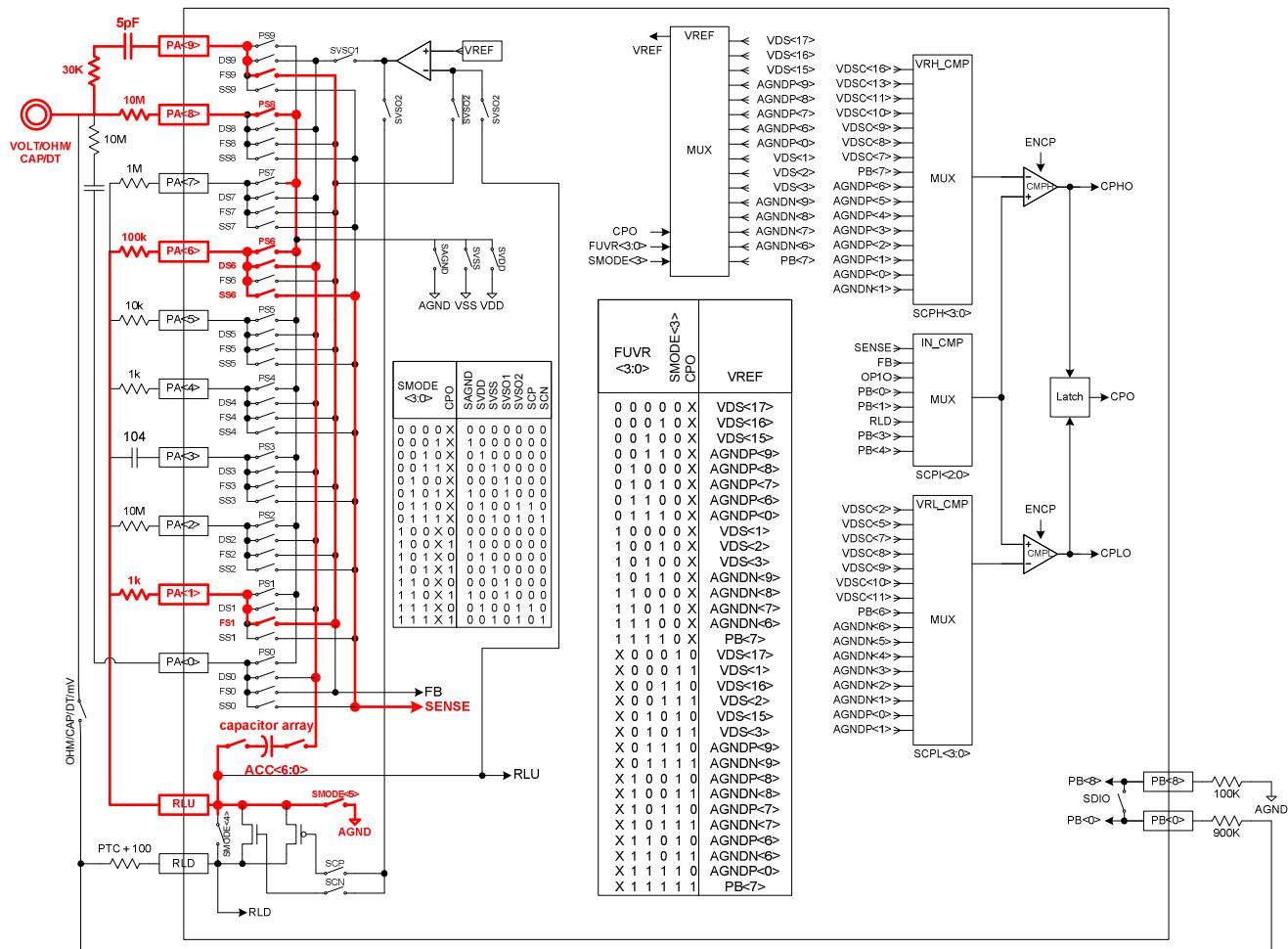

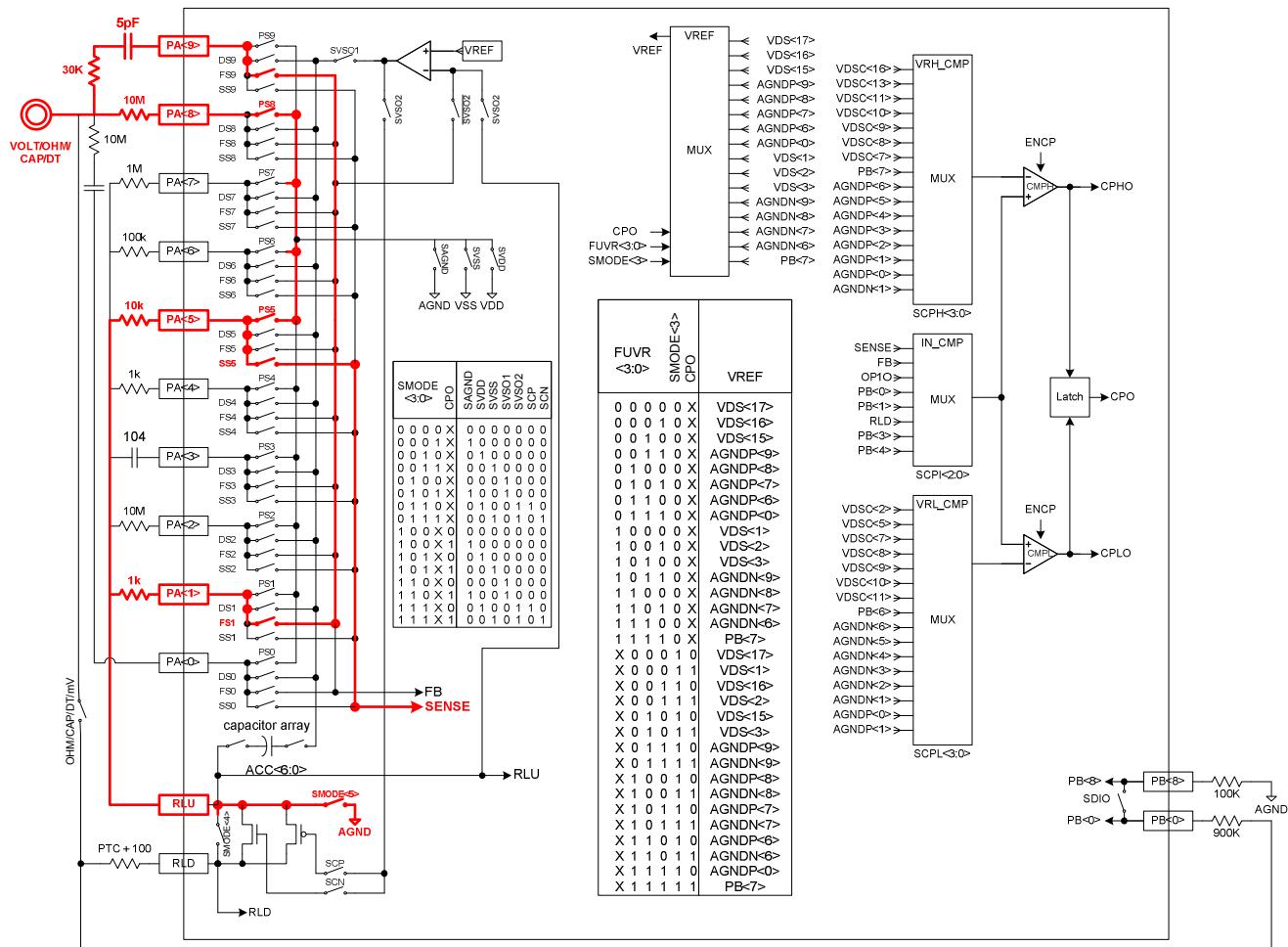
### 4.4. 500V Input Network Configuration


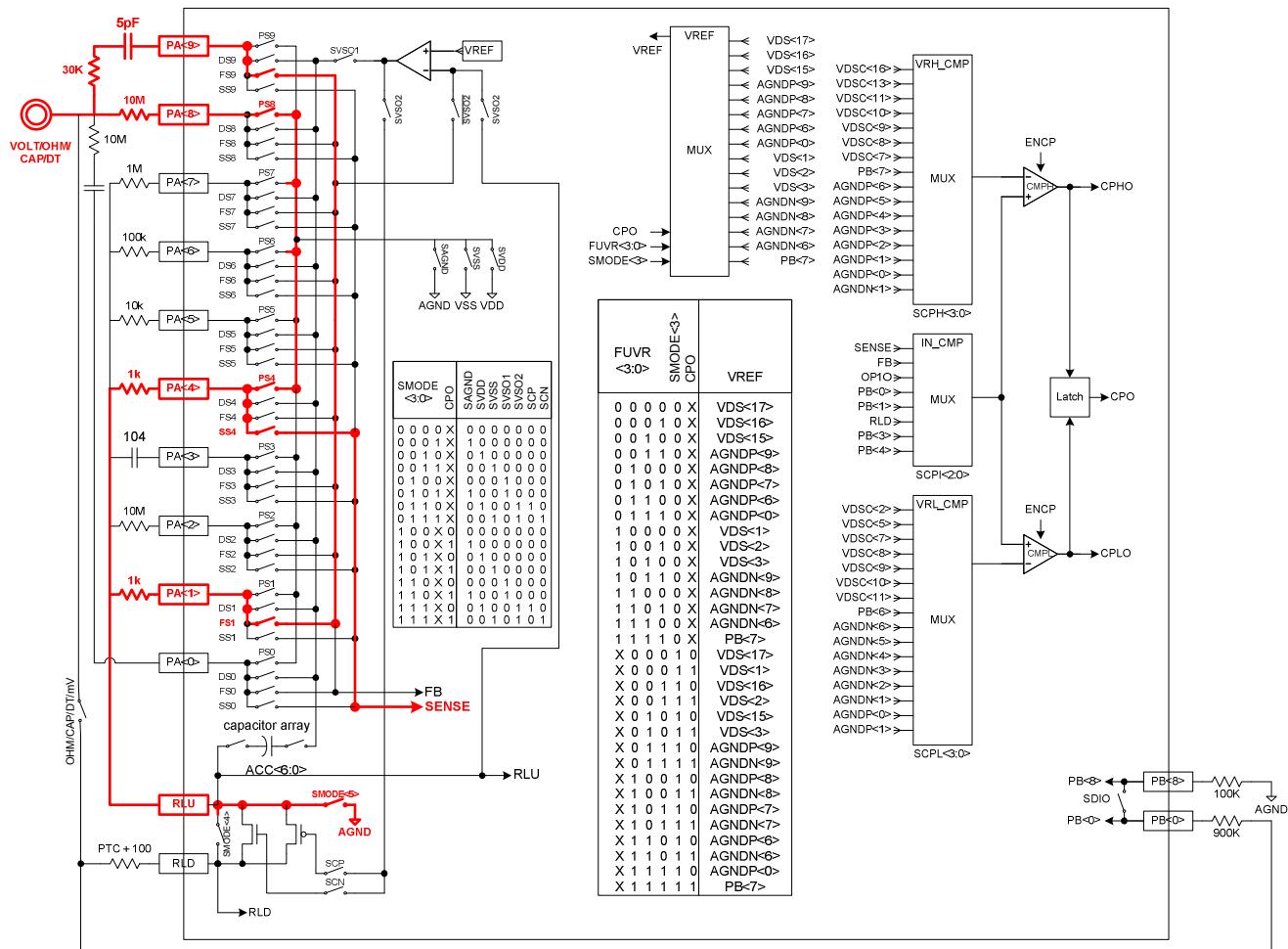
### 4.5. 1000V Input Network Configuration



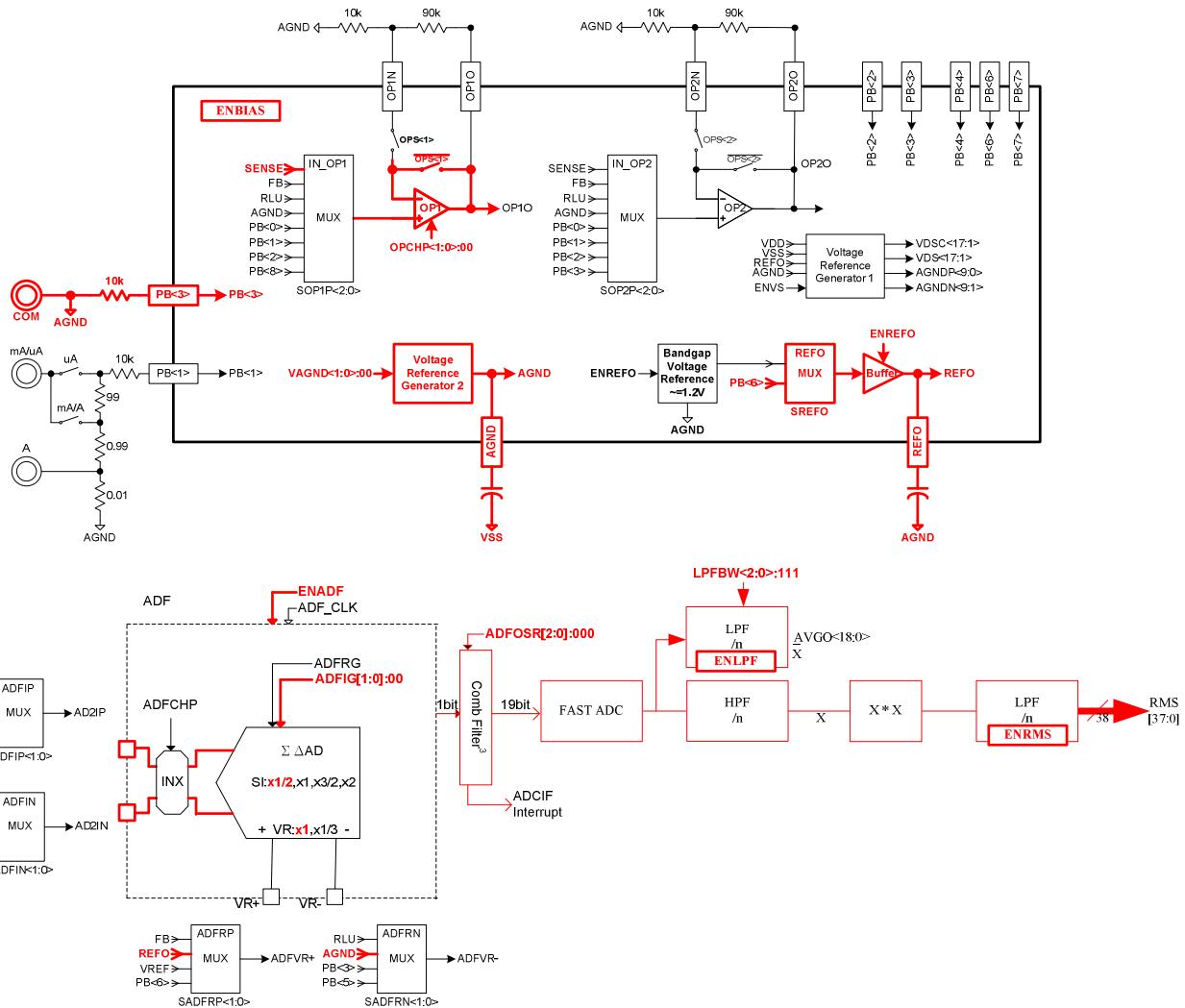
### 4.6. AC5V~1000V Measurement Network Configuration


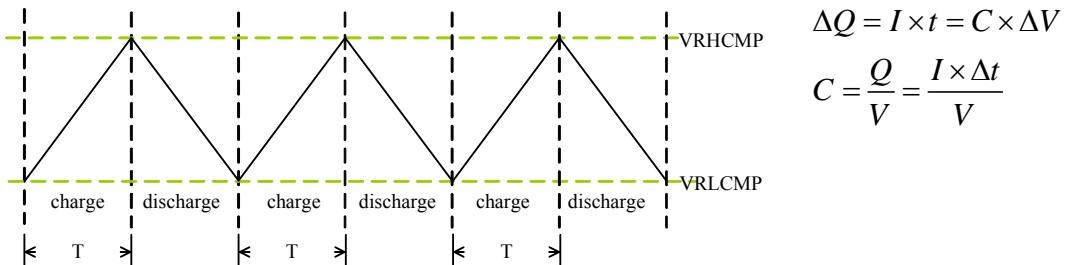
### 5. Capacitor


There are two ways to measure capacitor, constant voltage and constant current output mode. Under low capacitor ( $<1 \mu F$ ), users need to use constant voltage output mode for testing whereas using constant current output mode to test high capacitor ( $>1 \mu F$ ). Capacitor measurement uses charge/discharge test cycle to gain the value.




Capacitor measurement test procedure :

1. Select constant voltage (SMODE<7:0>=01110b) and constant current (SMODE<7:0>=11010b) test mode output.
2. Configure capacitor charge/discharge comparison voltage (VRHCMPP、VRLCMP) and the actual charge/discharge of capacitor is decided by comparator, ACPO.
3. Configure CTA<23:8> initial value of Frequency Counter. When INTF2 register, CTF bit is 1, CTC<23:0> divided by CTB<23:0> to gain the cycle length.

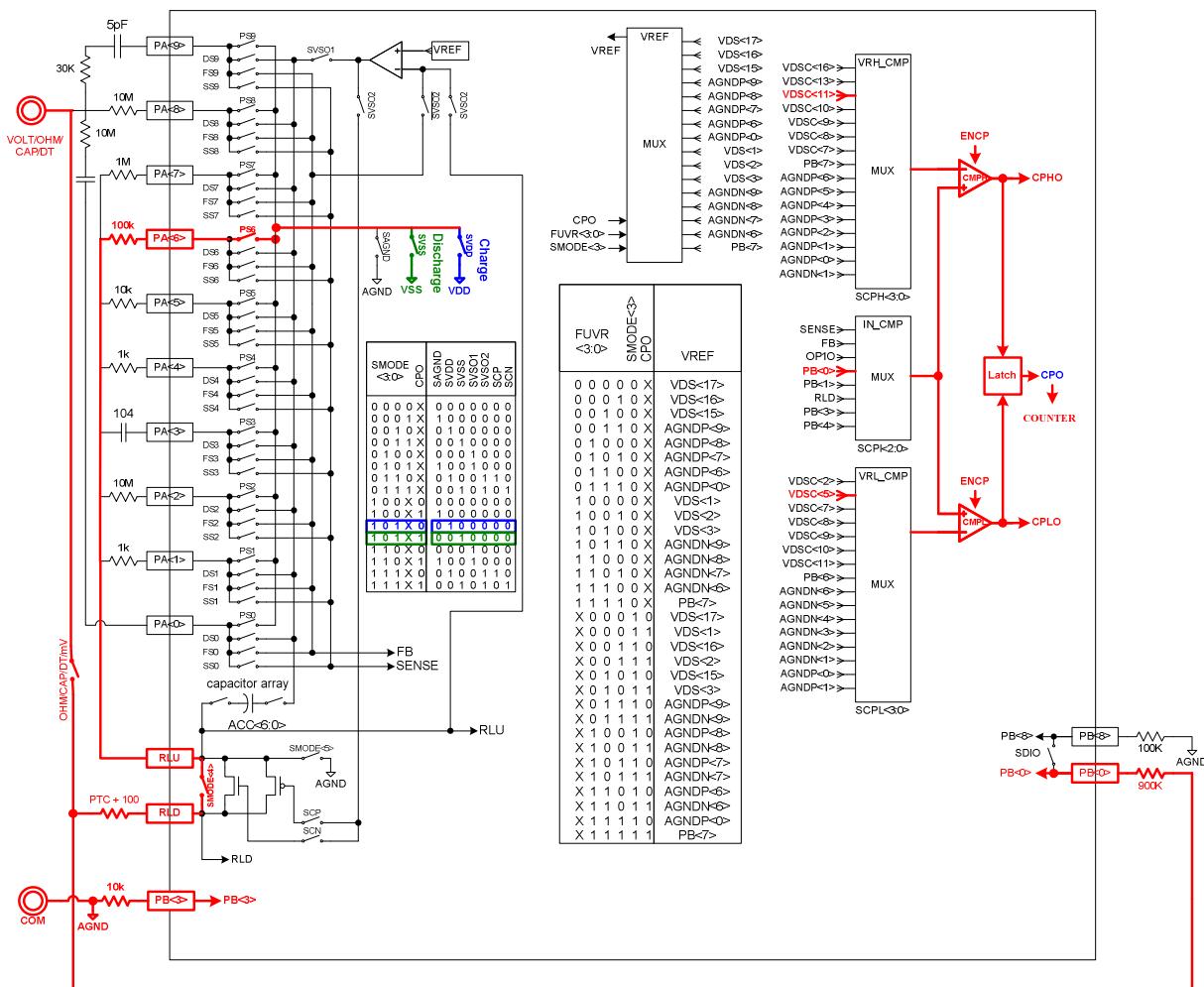
### 5.1. 50-500nF (Constant Voltage Charge/Discharge Measurement)



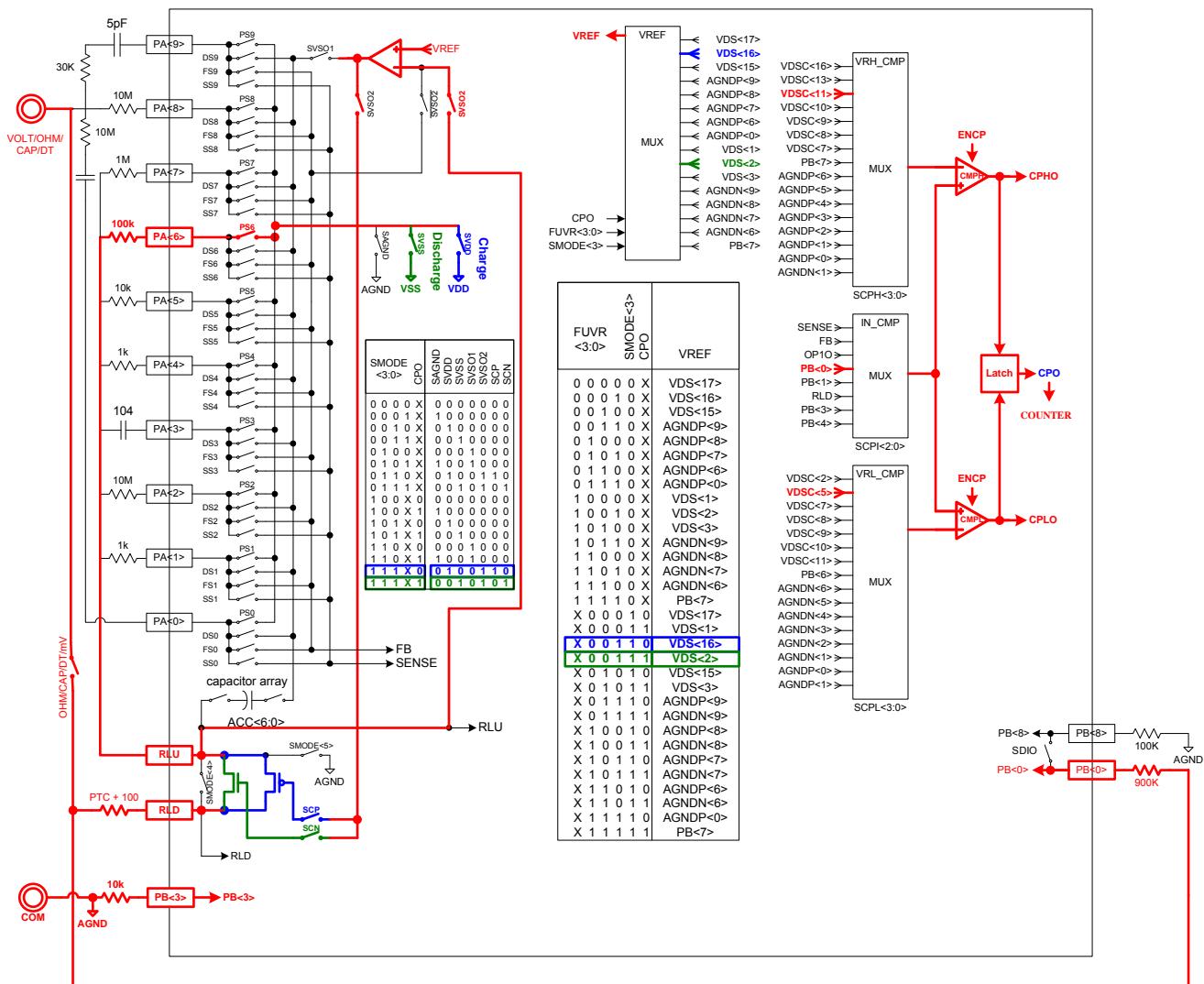
### 5.2. 5uF-50uF (Constant Current Charge/Discharge Measurement)



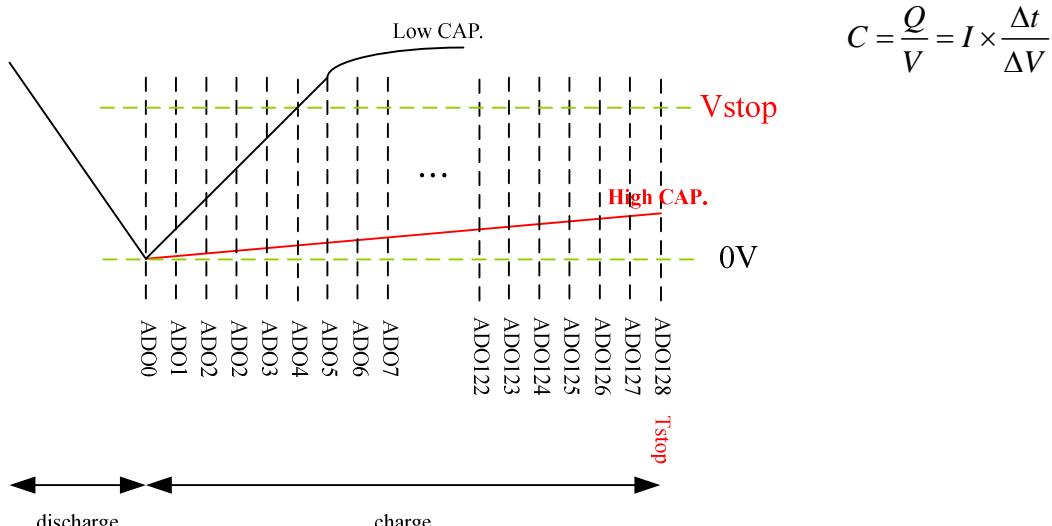
500uF~50mF capacitors require longer charge/discharge time, the only change of different ranges is the output current. Users can take the voltage difference under a fixed time ( $t$ ) to gain capacitor value. The change of capacitor value and voltage value is an inverse ratio.




### 5.3. 500uF(Charge)

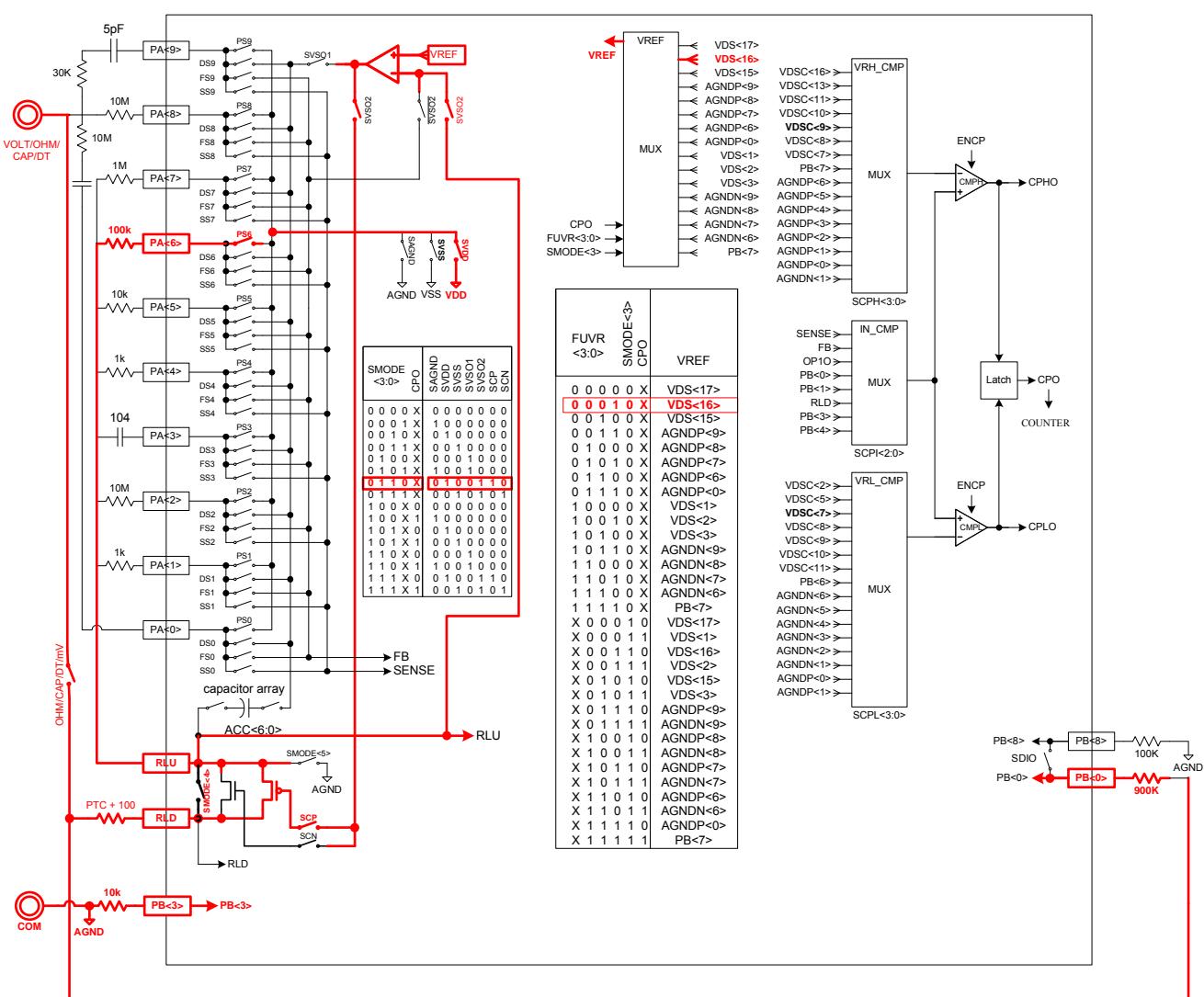


### 5.4. 5mF-50mF(Charge)

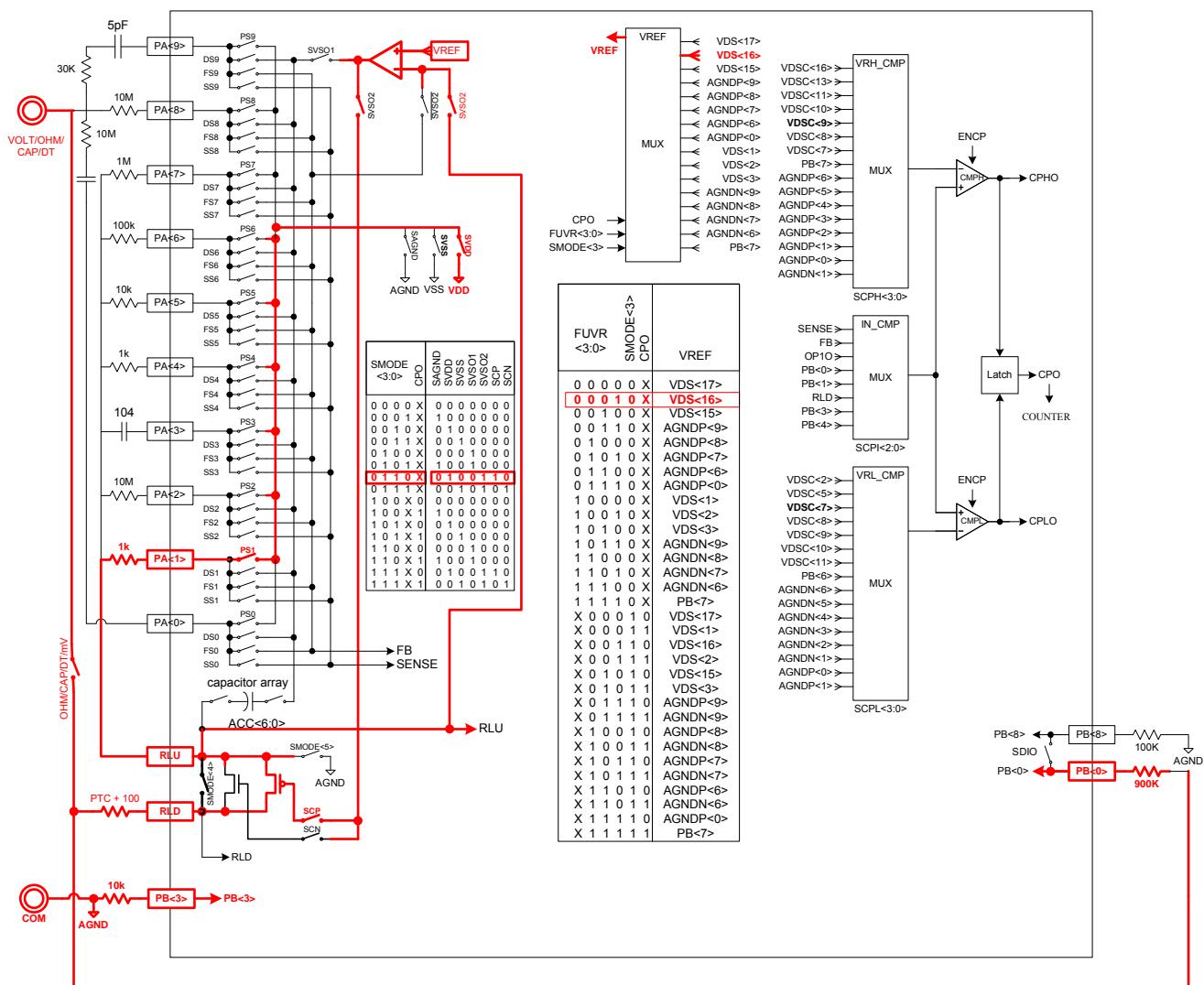

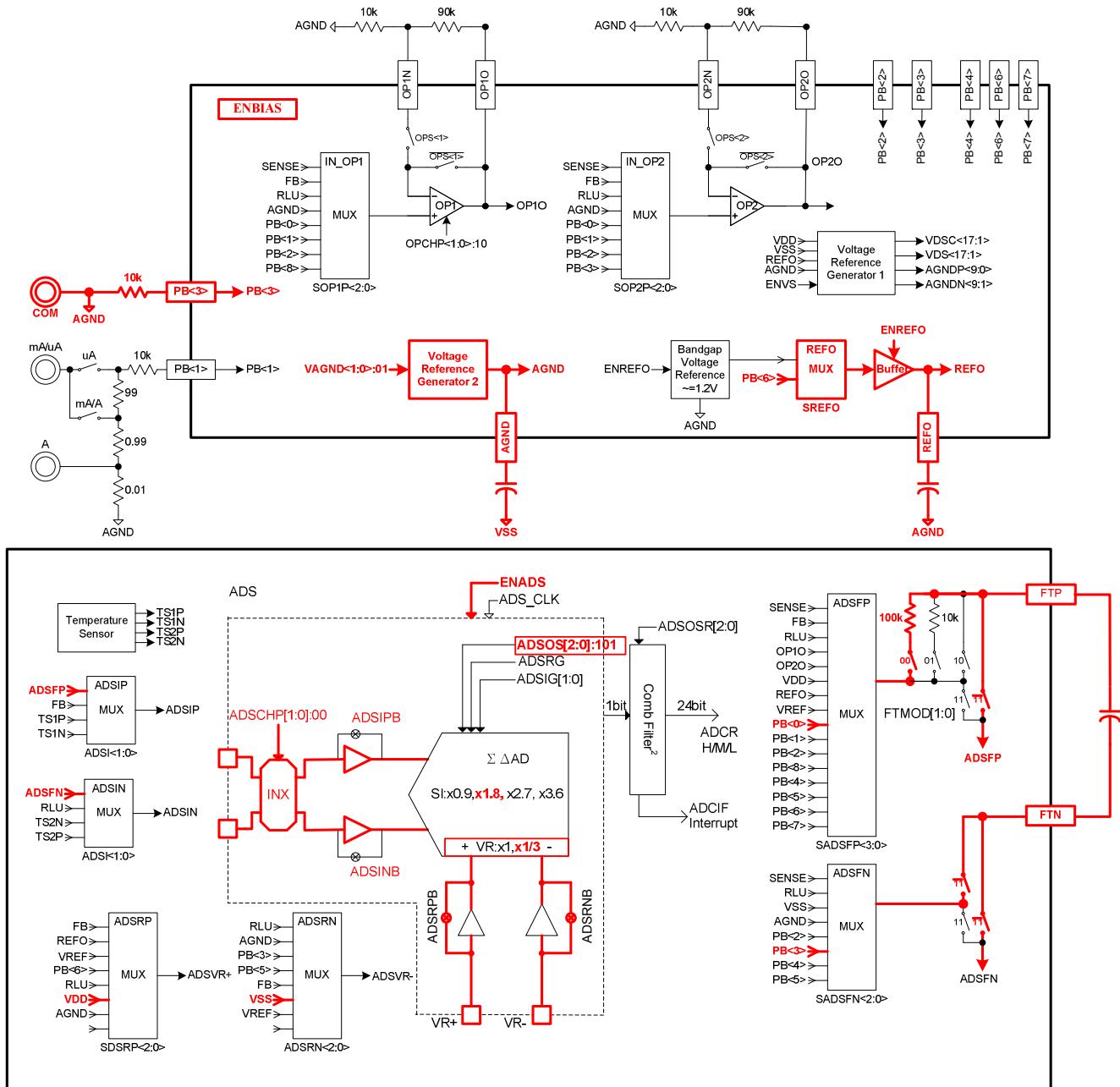
### 5.5. 500uF~50mF Measurement Network Configuration



### 5.6. Discharge (500uF~50mF)

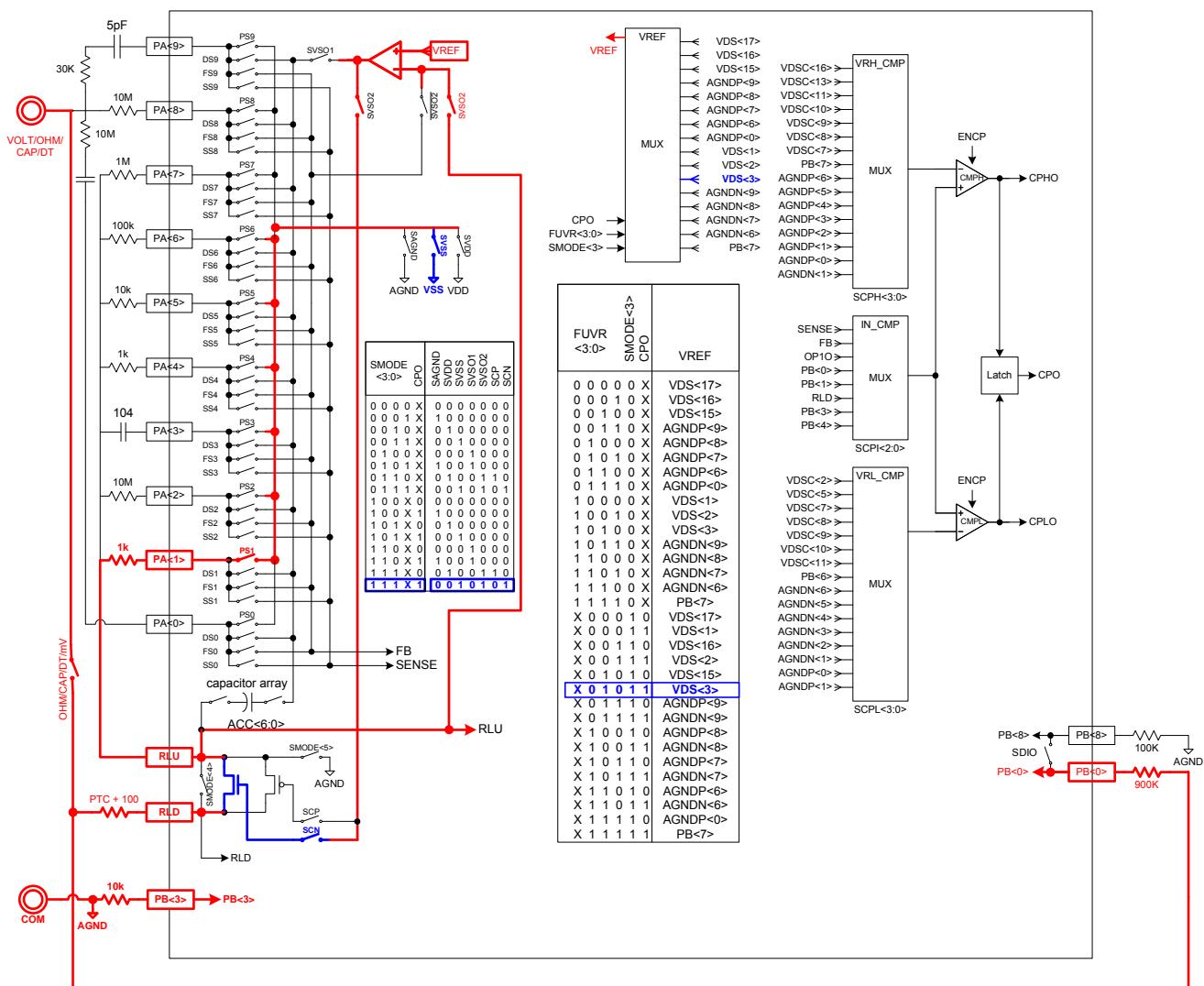


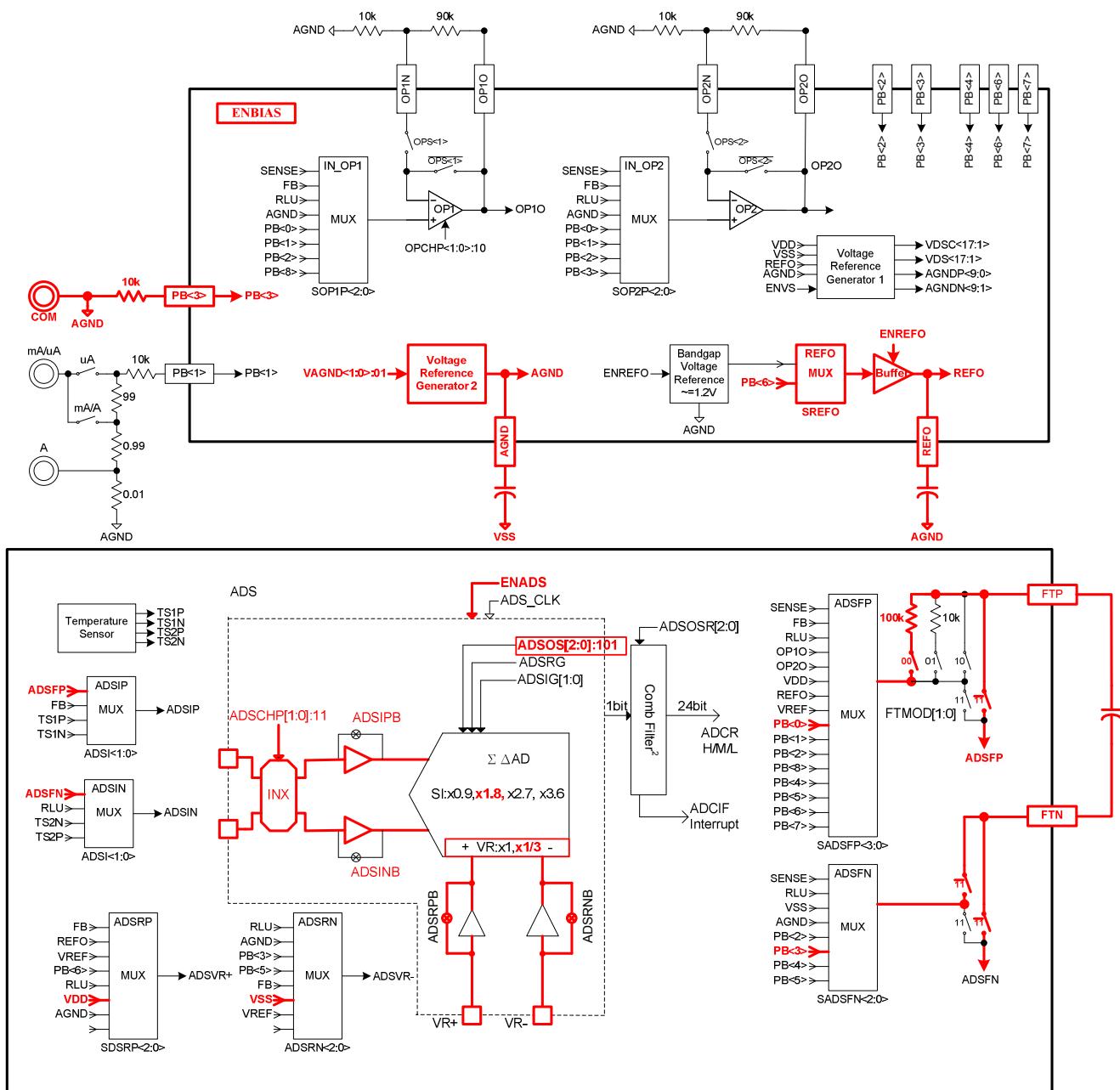
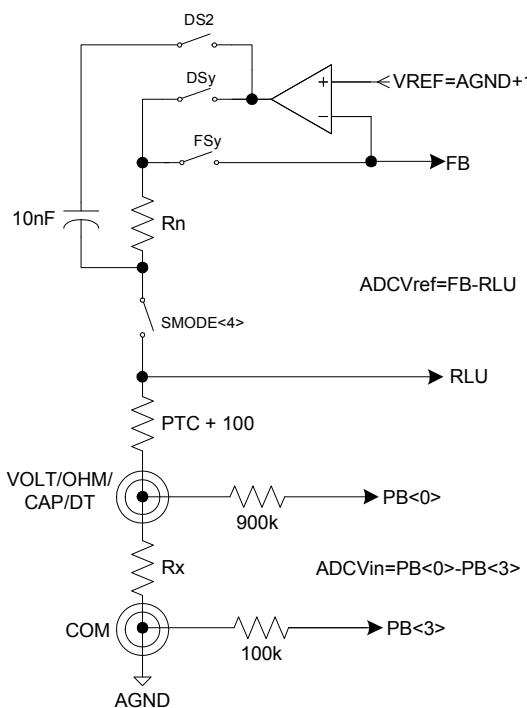
## 6. Resistor

The chip offers two ways to measure resistor, constant voltage and constant current measurement and different methods lead to diverse results.

Constant voltage or ratio resistor measurement design must input ADC signal and open reference voltage input buffer when measuring high resistor.  $3M\Omega$  parallel connection impedance will be generated if ADC input was not opened. It is suggested to use constant current resistor measurement when design  $500k\Omega$  to  $50M\Omega$  application. The measurement equation is given below :




$$I_{Rx} = I_{Ry}$$

$$V_{Rx} = I_{Rx} \times Rx = \frac{V_{Rn}}{Rn} \times Rx$$

$$R_{READ} = \frac{V_{Rx}}{V_{Rn}} \times Full\ Scale = \frac{ADCV_{in}}{ADCV_{ref}} \times Full\ Scale$$

Constant current resistor measurement design has higher internal impedance of DSn and SVDD electrical switches; it will have parallel connection with Rn resistor and to cause output current deviation. It is recommended to use constant voltage resistor measurement when designing 500k $\Omega$  or below applications. The measurement equation is given below :

# HY313X Configurations

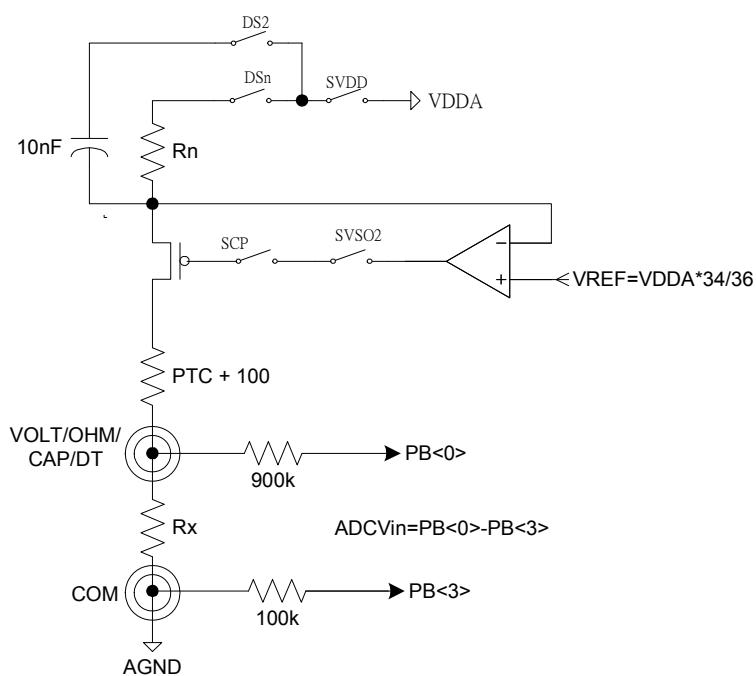


$$I_{Rx} = I_{Rn} = \frac{VDDA - VREF}{Rn}$$


$$R_{READ} = \frac{ADCV_{in}}{ADCV_{ref}} \times Full\ Scale$$

$$R_{READ} = \frac{Rx \times I_{Rx}}{ADCV_{ref}} \times Full\ Scale$$

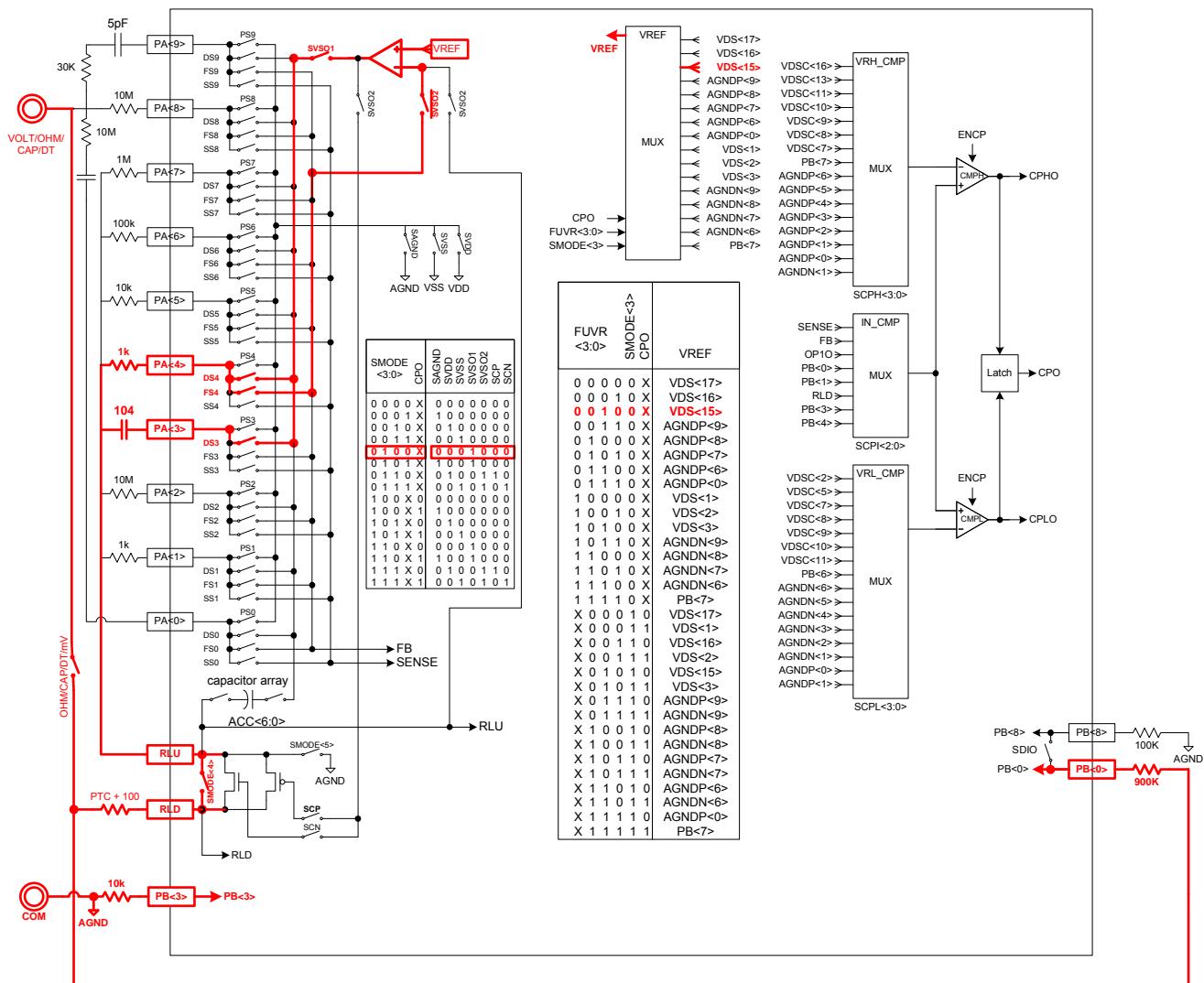
### 6.1. 50ohm/500ohm Input Network Configuration



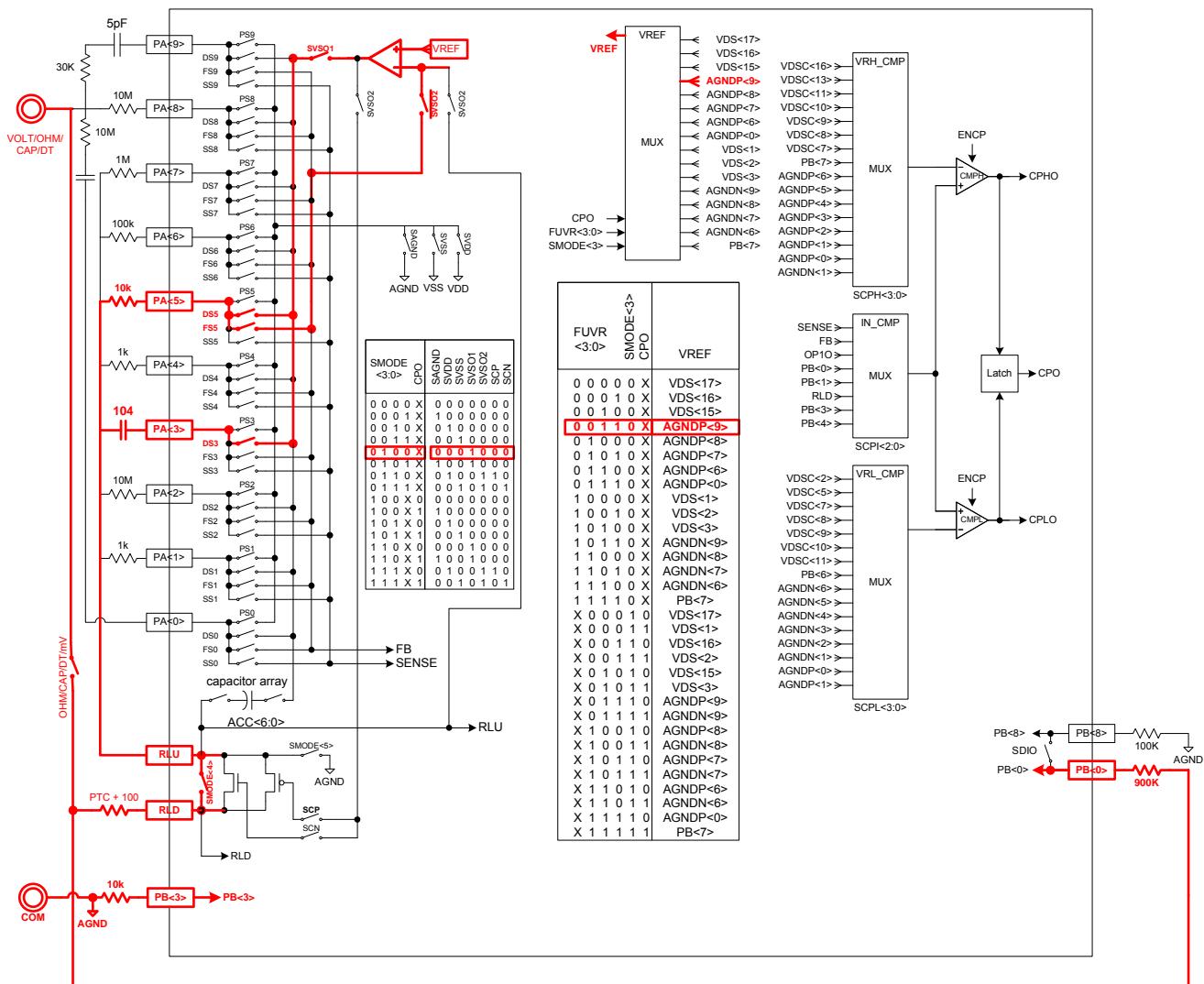
### 6.2. 5K ohm Input Network Configuration



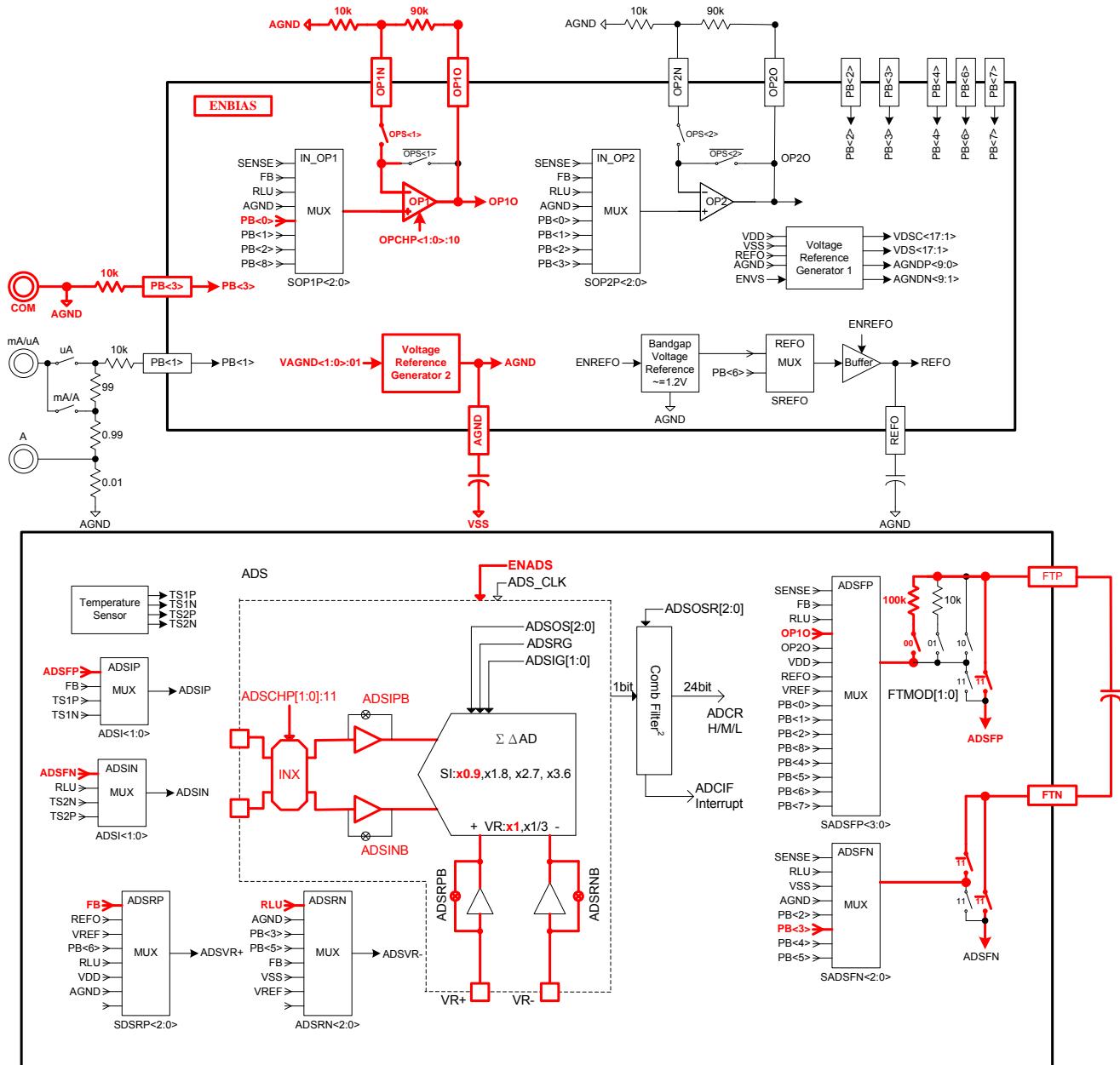
### 6.3. 50ohm Measurement Network Configuration



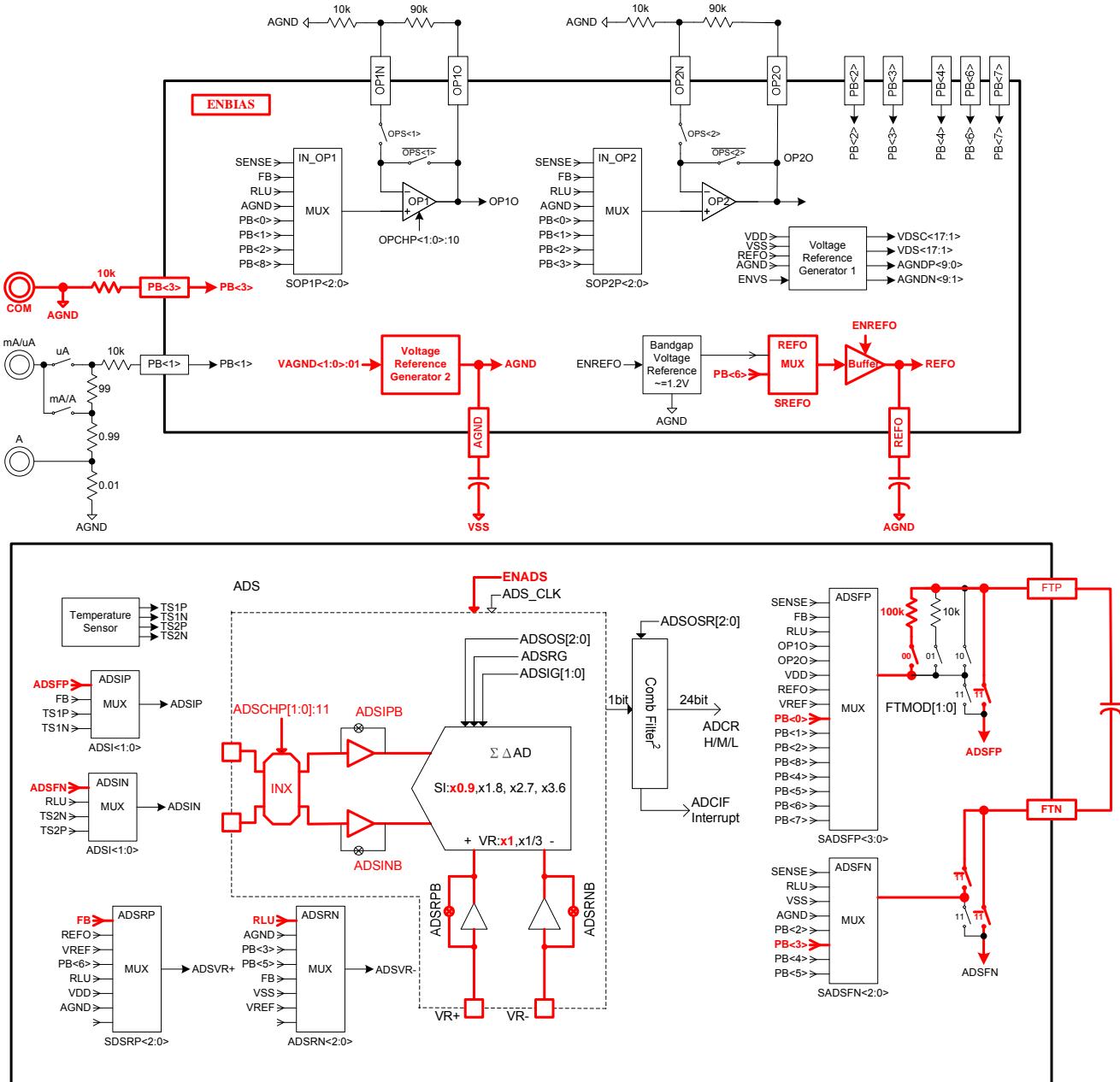
#### **6.4. 500 ohm~50K ohm Measurement Network Configuration**



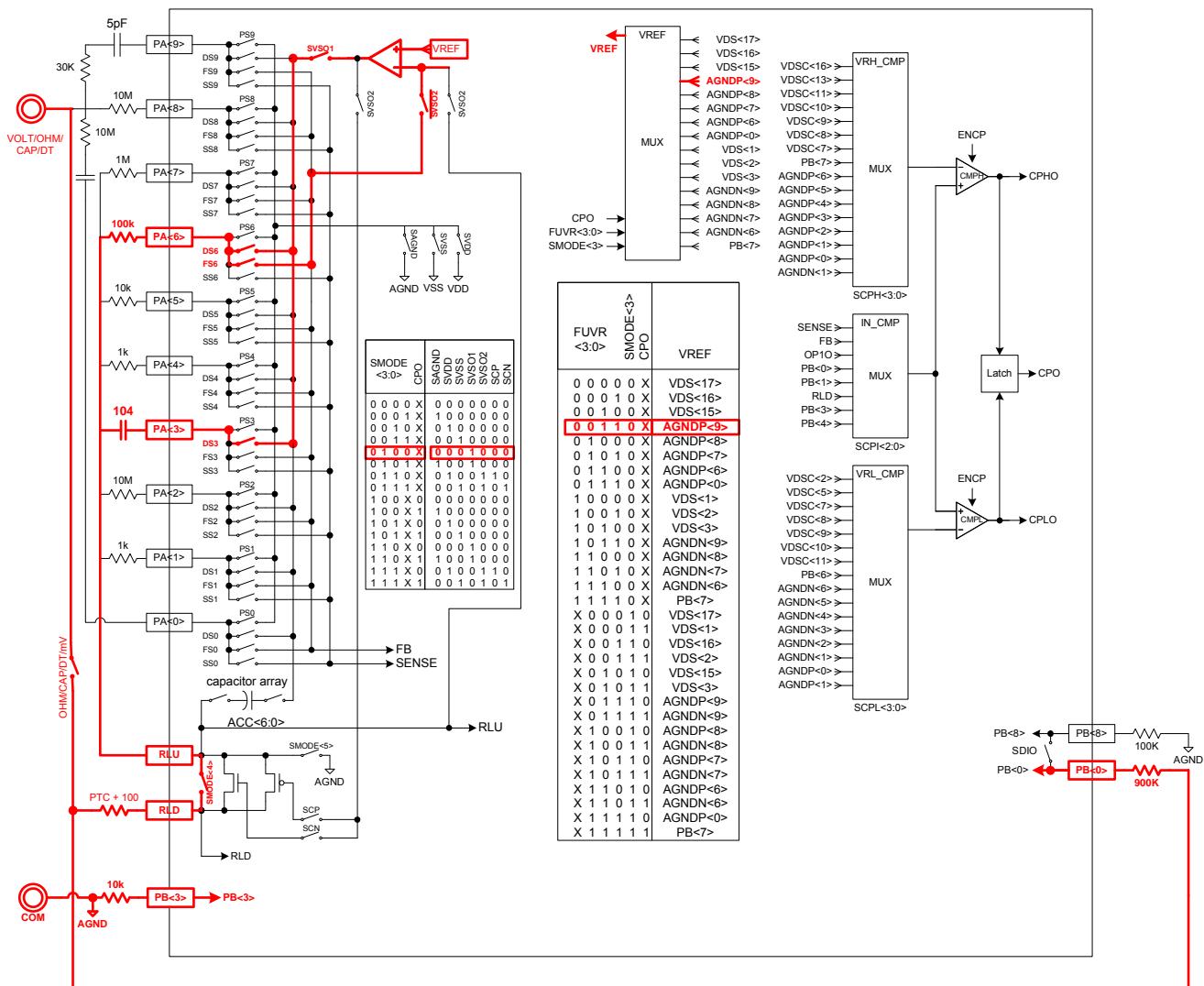
## 6.5. 50Kohm Input Network Configuration



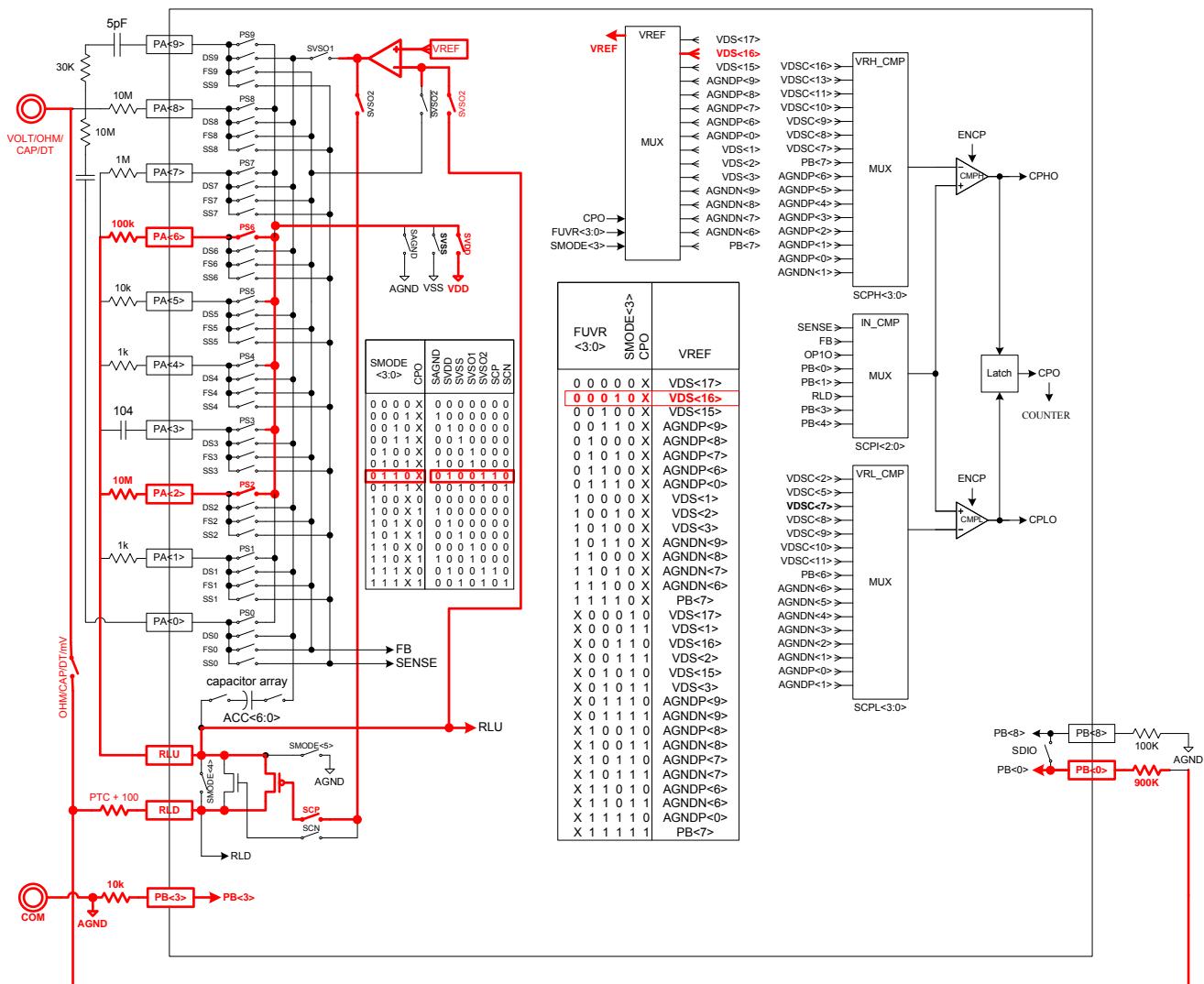
## 6.6. 500Kohm Input Network Configuration




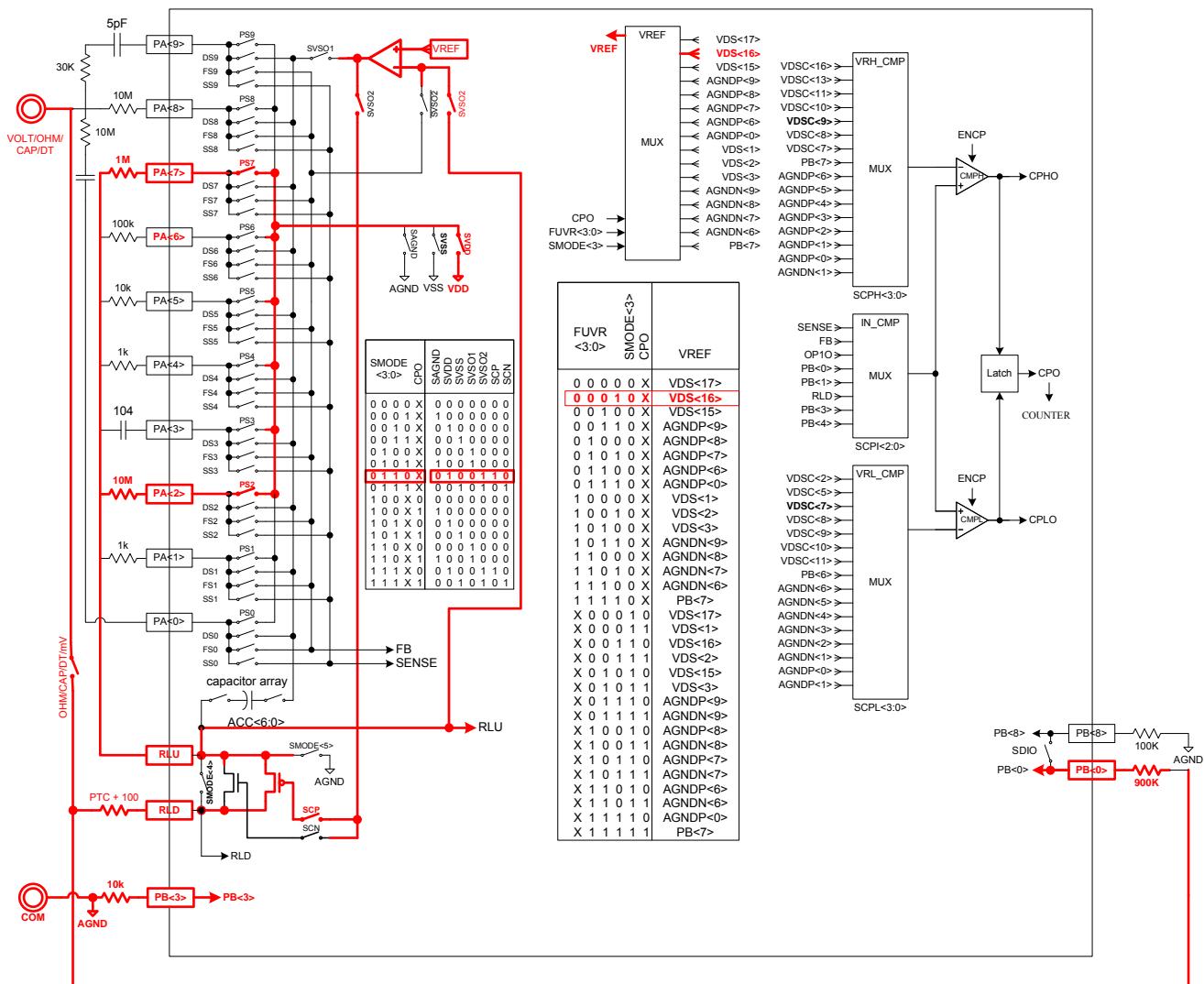
### 6.7. 5M ohm Input Network Configuration


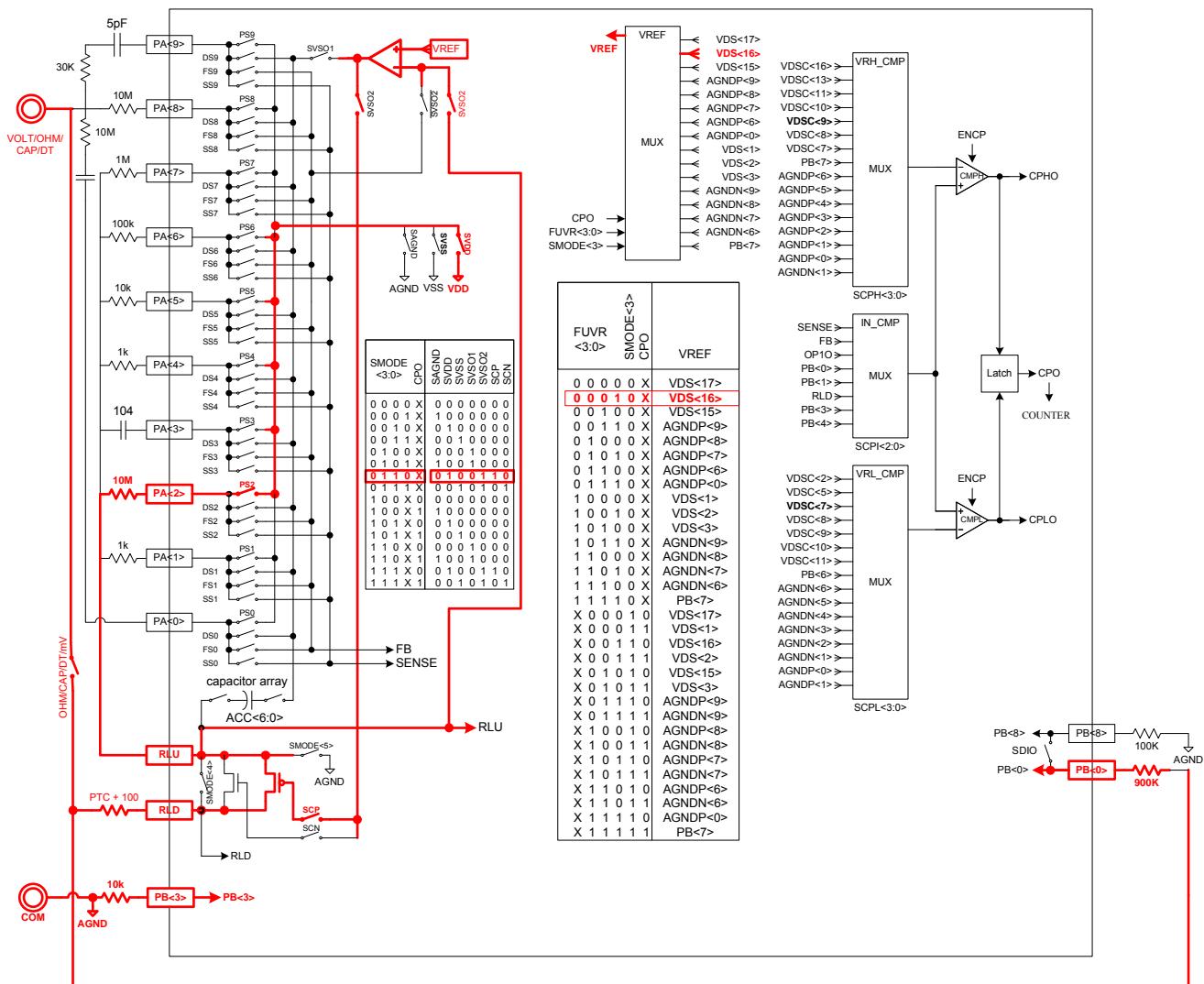
### 6.8. 50Mohm Input Network Configuration


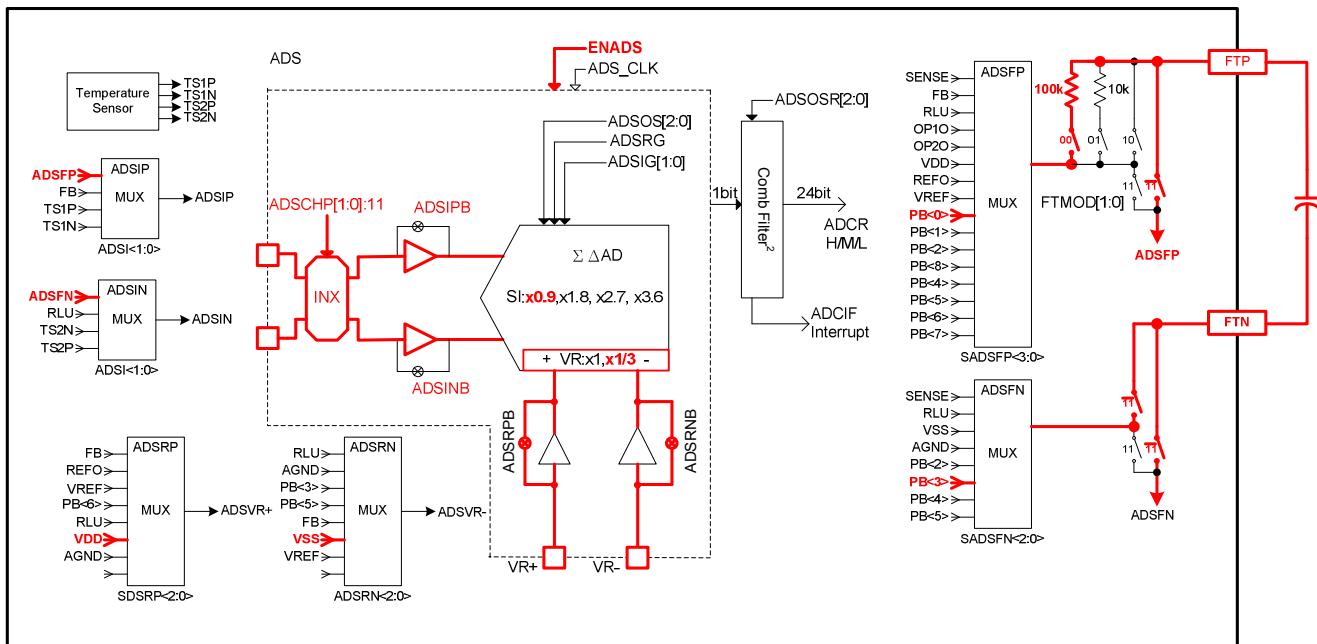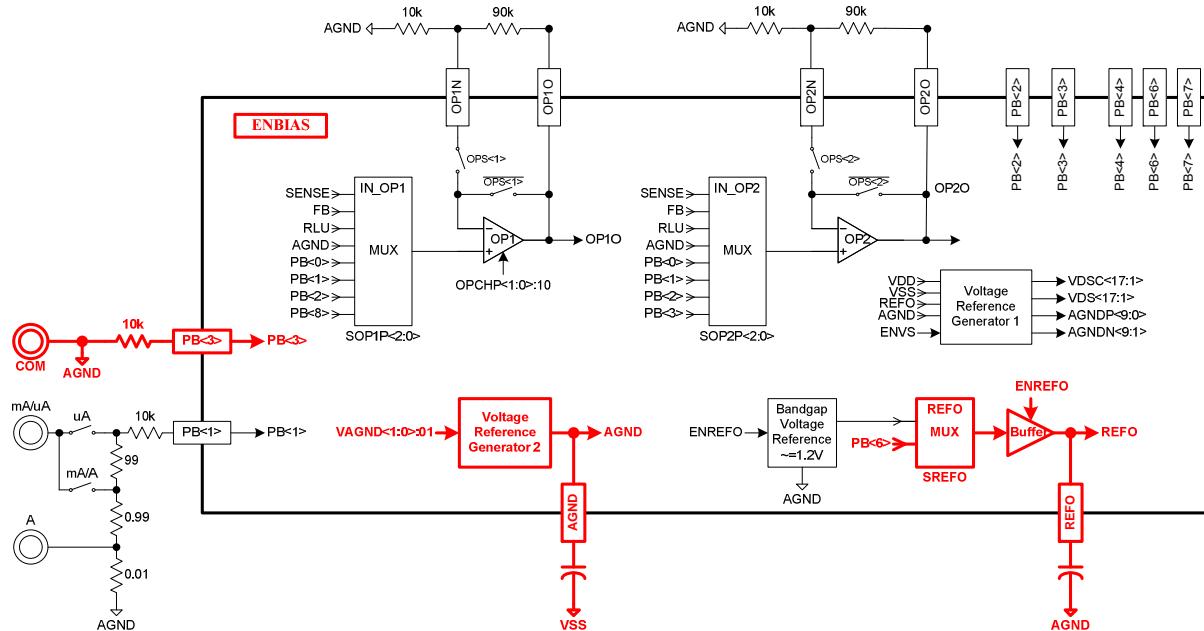
## 6.9. 500Kohm~50Mohm Measurement Network Configuration




### 7. Diode


Diode function is to measure Forward Voltage or called PN Barrier Potential. This chip offers positive/negative constant current source or positive/negative constant voltage source measurement. This example illustrates positive constant current measurement.

When constant current passed through diode, both edges of component will have voltage difference. The voltage is around 0.2V~1.5V, to prevent exceeding full scale. Thus, taking  $900\text{k}\Omega$  and  $100\text{k}\Omega$  to form 10 times attenuation.
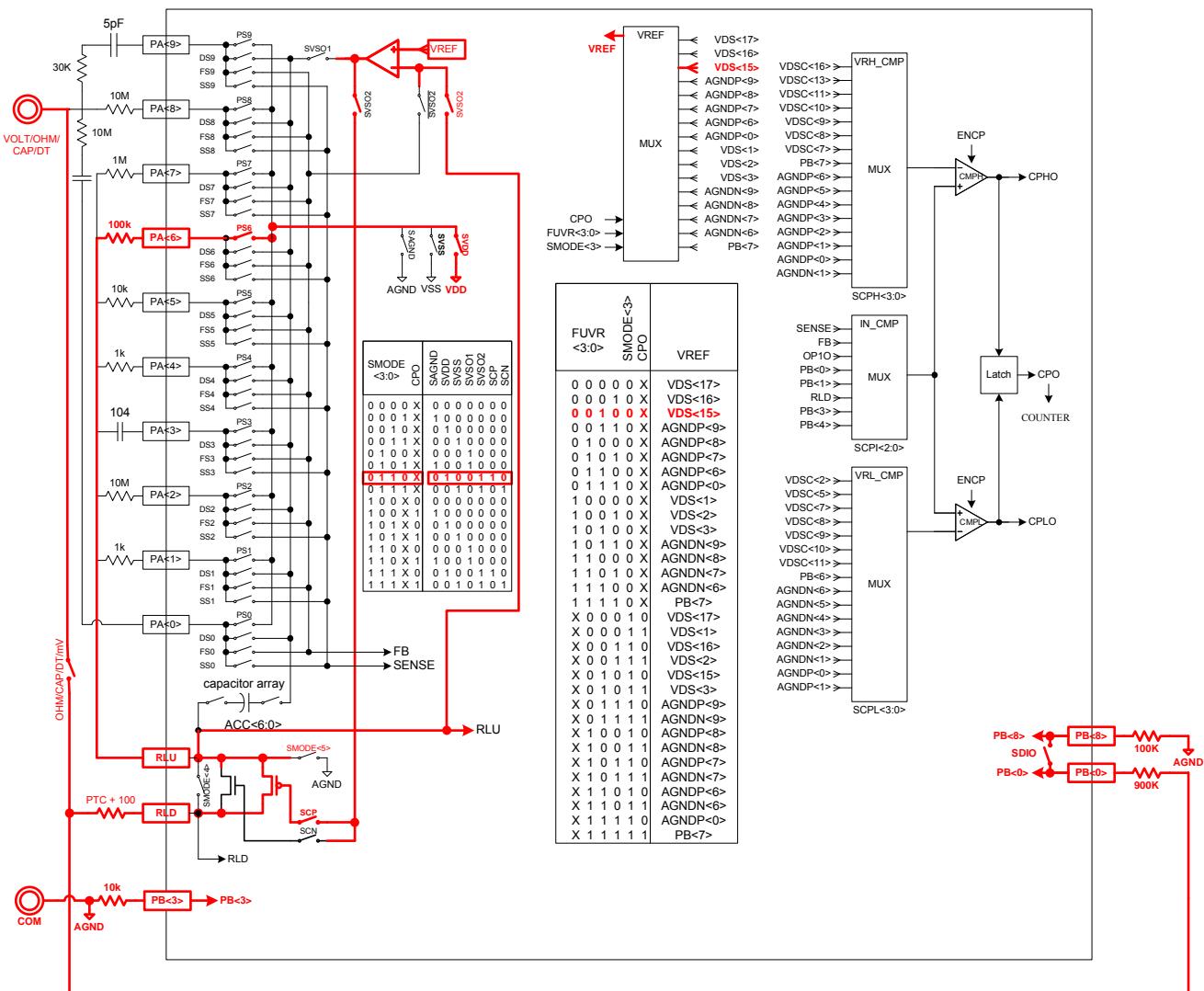
#### 7.1. Diode Input Network Configuration



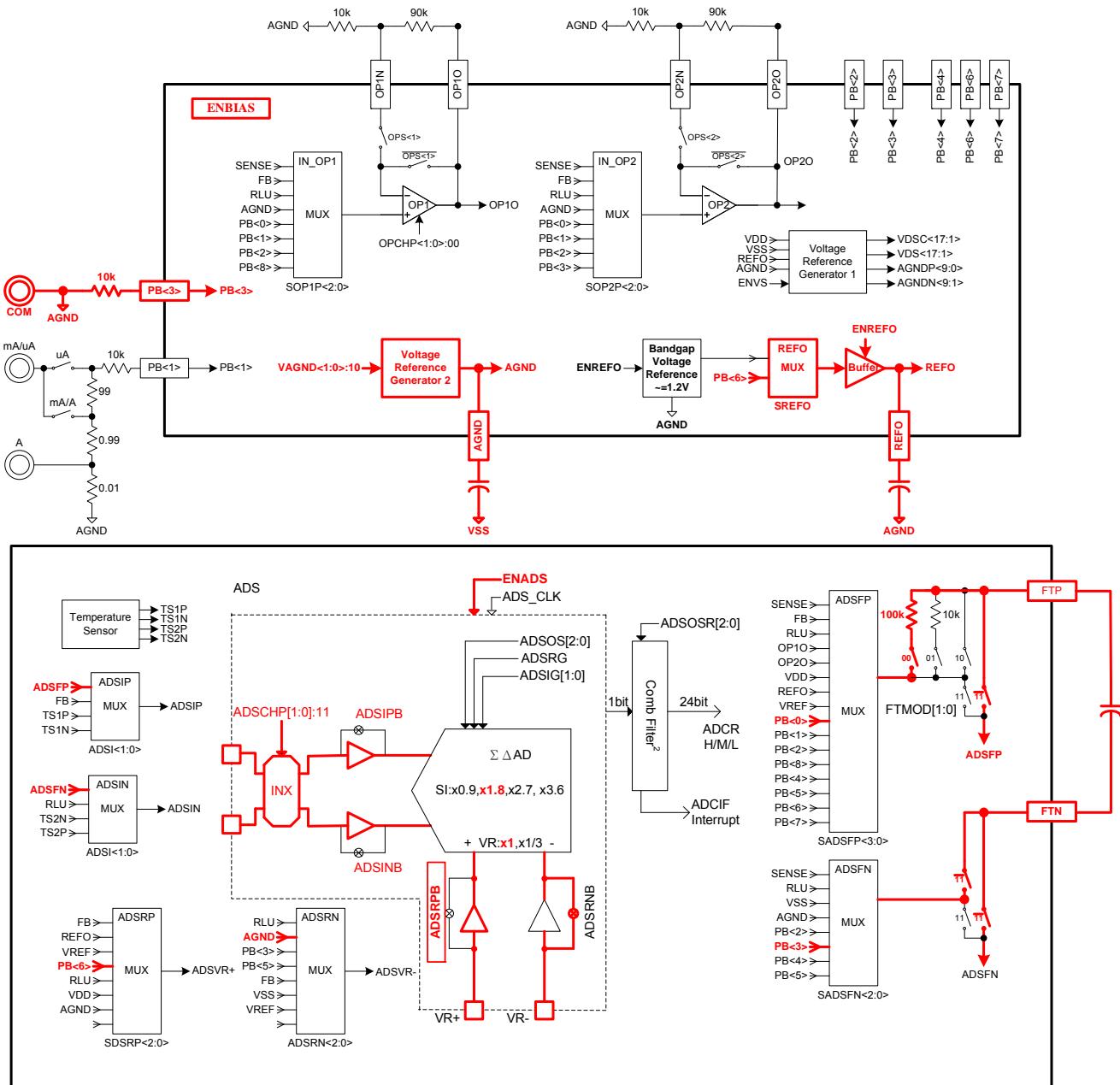
### 7.2. Diode Measurement Network Configuration


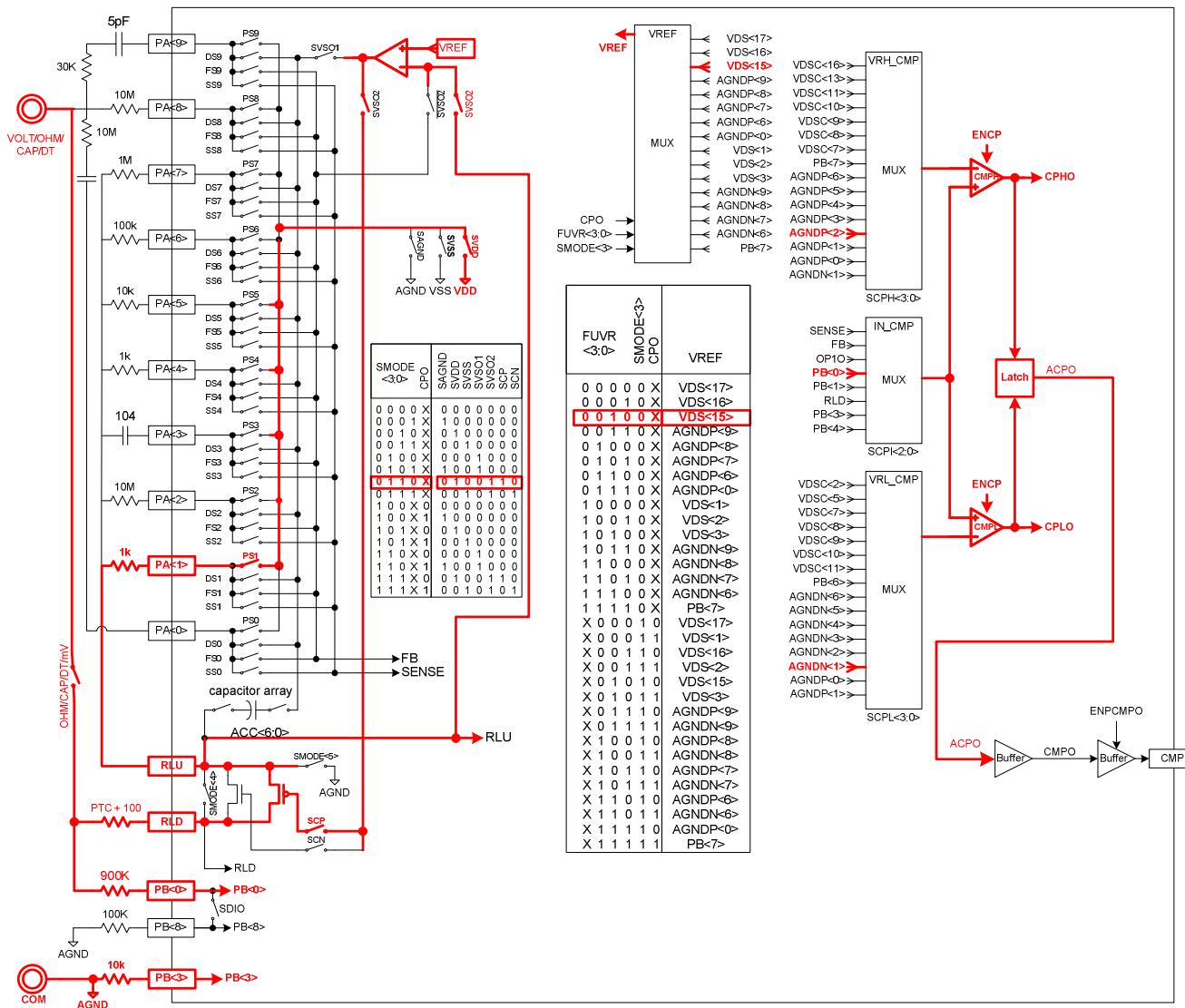
## 8. Continuity


This function can use constant current or constant voltage output measurements. This case is positive constant current output measurement.





## 9. Current

Current measurement is similar with that of measuring mV.


## 9.1. DC 50mA

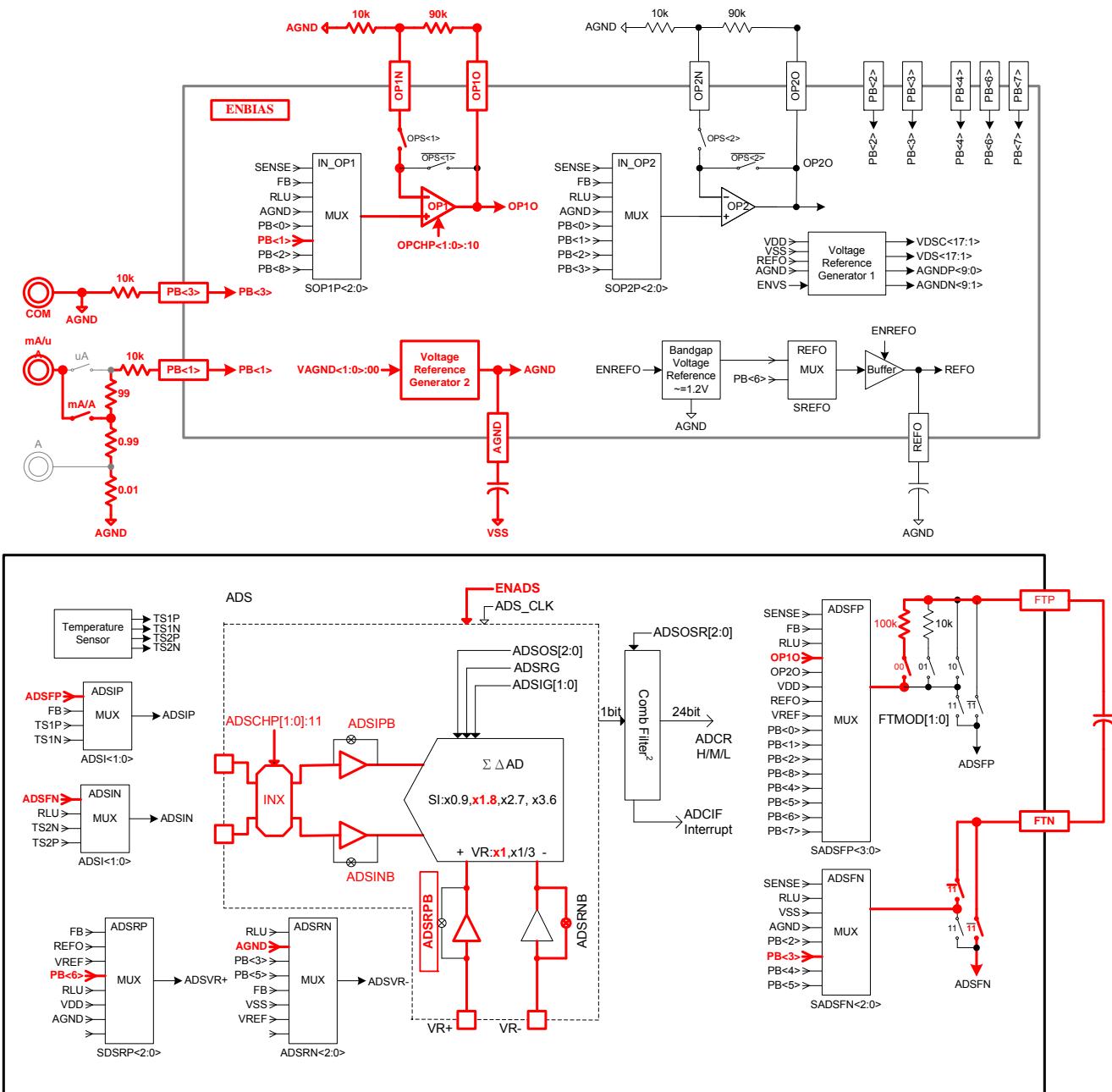


### 9.2. DC 500mA

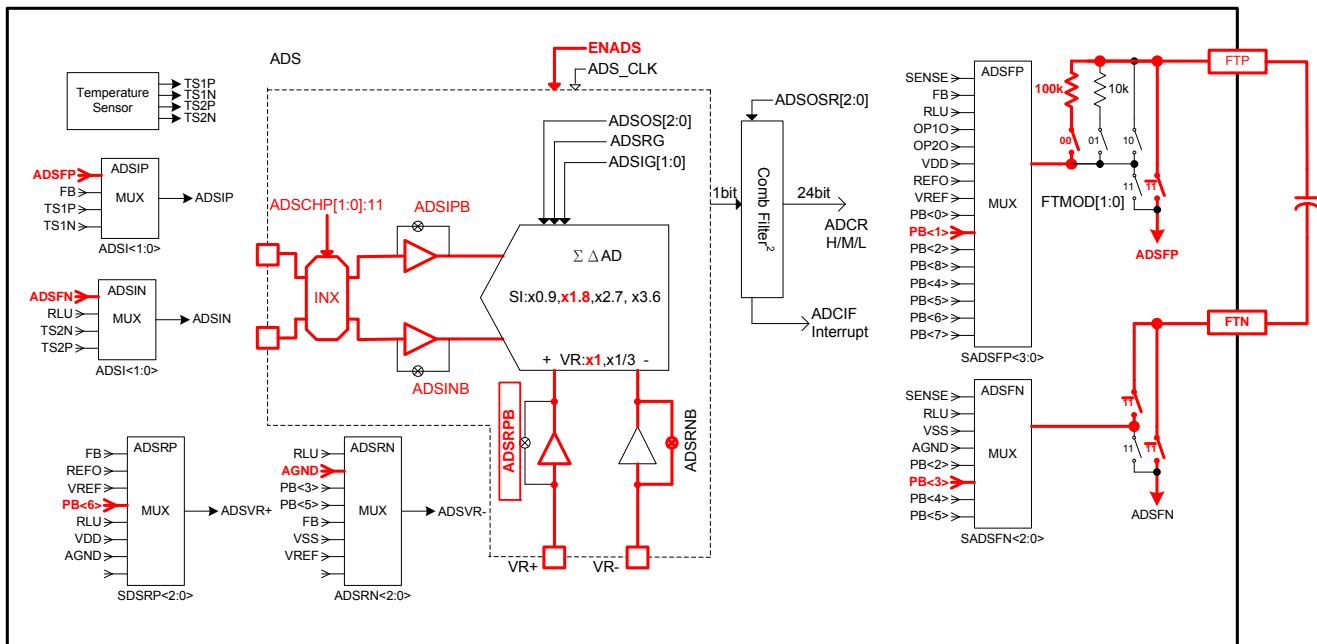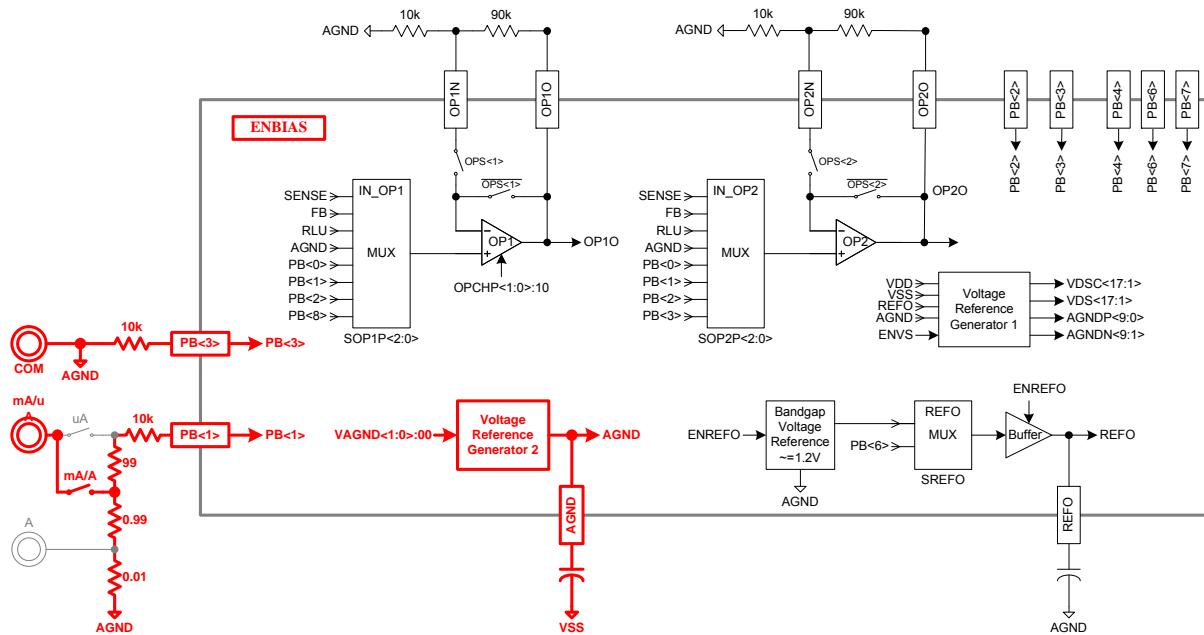

### 9.3. AC 50mA

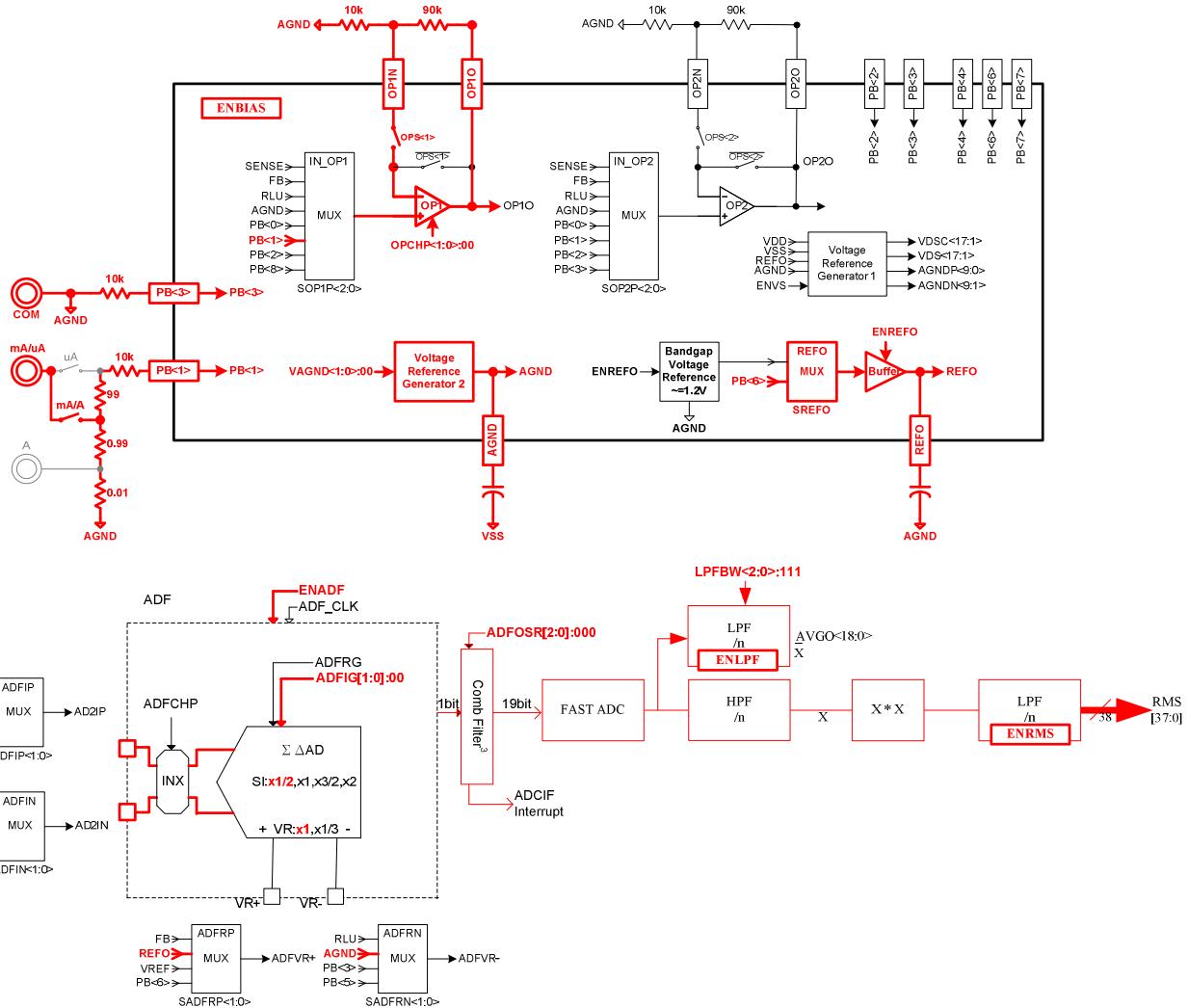


### 9.4. AC 500mA

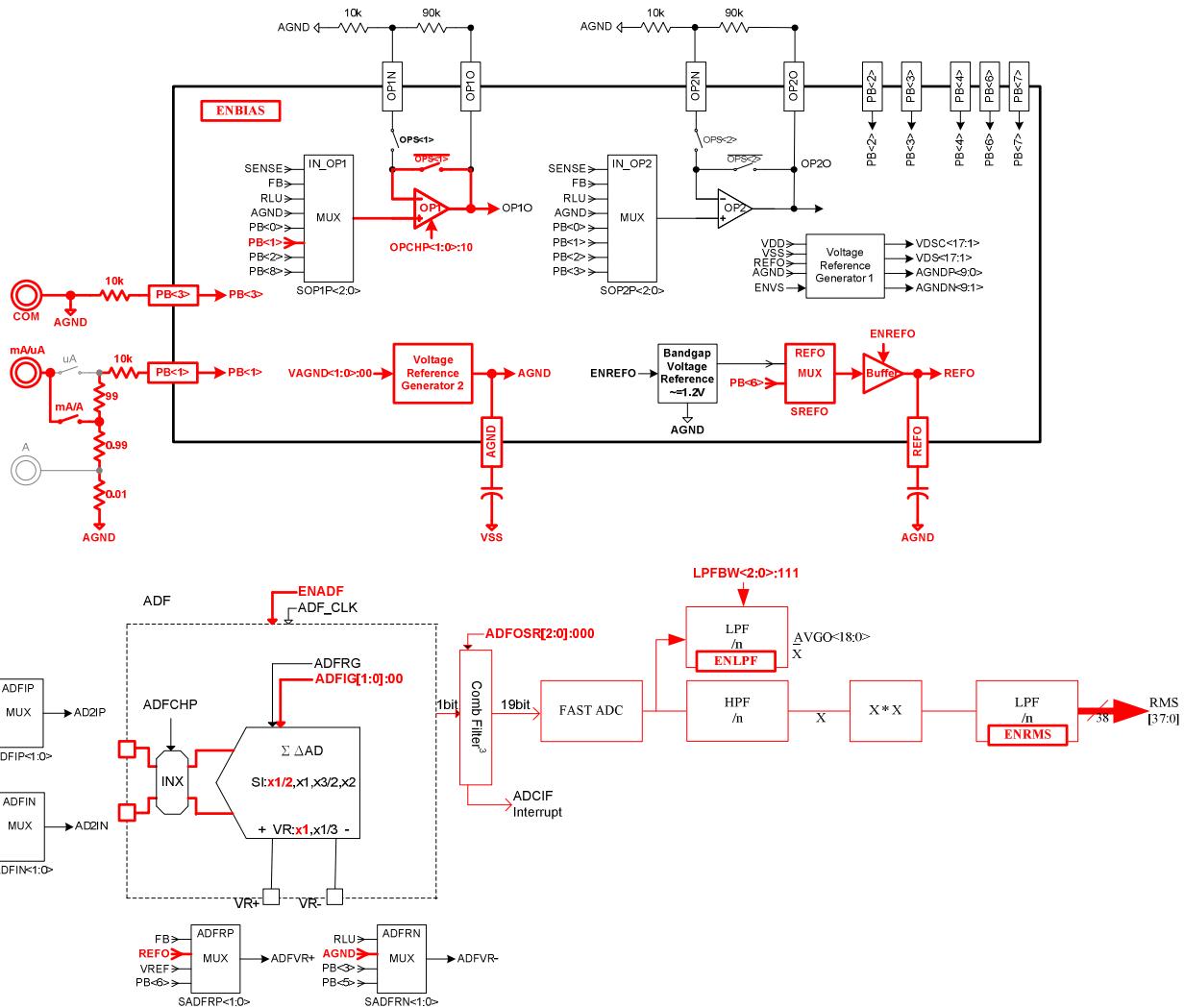


### 10. Frequency
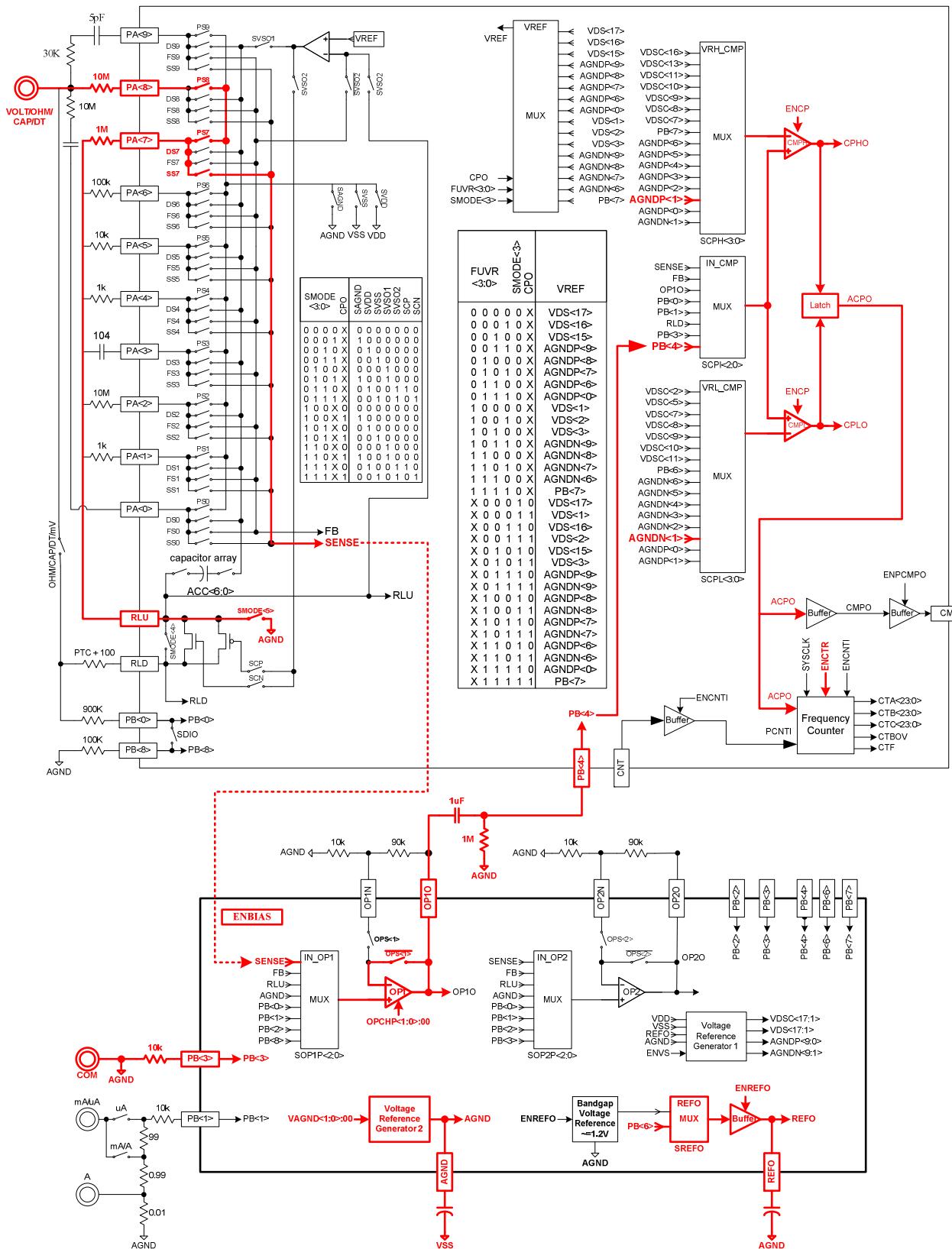
#### 10.1. Voltage input

When measured frequency, the signal is inputted by PA<n> and PB<n>. If the input contains DC, must be removed by AC Coupled capacitors.



## 10.2. CNT input

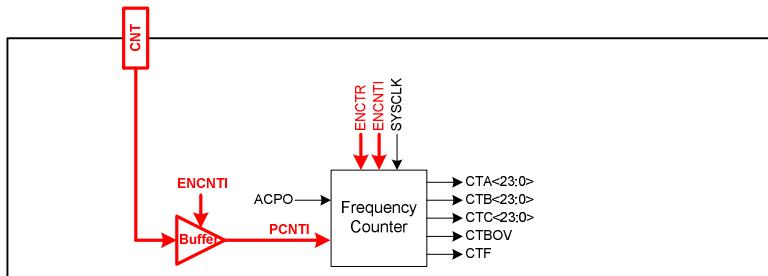

### **11. Revision History**

Major differences are stated thereafter:

---

Version	Page	Revision Summary
V01	All	First edition
V02	All	Revise all contents